

**CHAPTER-2**  
AC CIRCUITS  
3-PHASE CIRCUITS


## Three Phase Balanced Systems

→ Polyphase - No. of phases are available.

→ Advantages:

- 1) More output
- 2) Smaller size.
- 3) 3-phase motors are self starting.
- 4) More power is transmitted.
- 5) Smaller cross-sectional area of conductors.
- 6) Better power factor.
- 7) Horsepower rating of motors and ~~the~~ KVA of transformers are higher.


→ Generation of Three phase EMF:

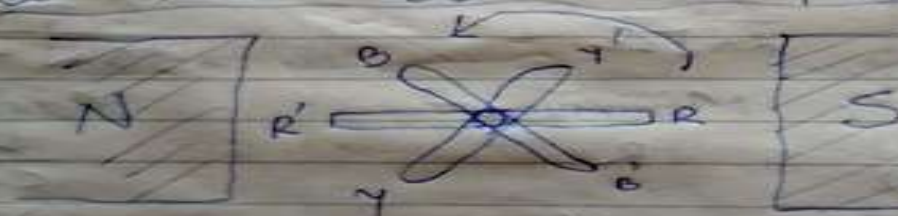


$$V_R = V_m \sin \omega t$$

$$V_Y = V_m \sin (\omega t - 120^\circ)$$
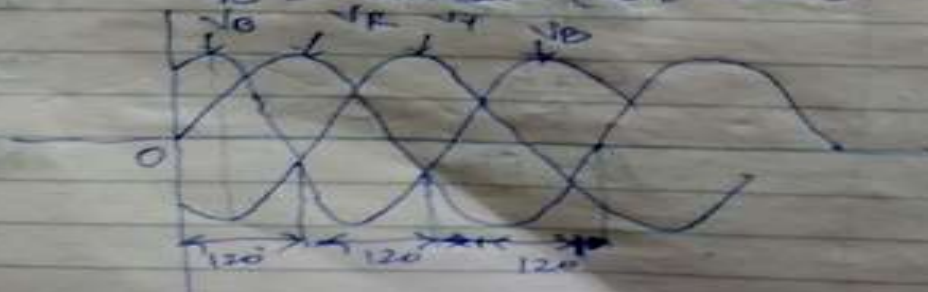
$$V_B = V_m \sin (\omega t - 240^\circ) = V_m \sin (\omega t + 120^\circ)$$



Phase representation

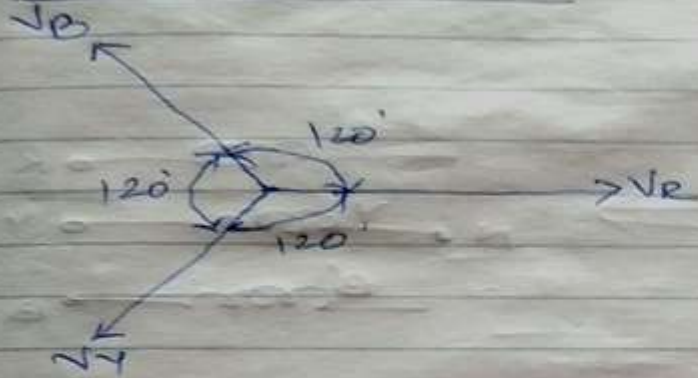

Vector addition of three phase voltages at any instant is zero.

$$\Rightarrow V_R + V_Y + V_B = 0$$

$$\text{LHS } V_R + V_Y + V_B$$

$$= V_m \sin \omega t + V_m \sin(\omega t - 120^\circ) + V_m \sin(\omega t + 120^\circ)$$

$$= (V_m + j0) + [V_m \cos 120^\circ - j V_m \sin 120^\circ] + [V_m \cos 120^\circ + j V_m \sin 120^\circ]$$

$$= V_m - \frac{V_m}{2} - \frac{V_m}{2}$$


$$= V_m - V_m$$

$$= 0$$


$V_R + V_Y + V_B = 0$

Types of Three phase Supply Connections

Three phase three wire (Wye) Connection

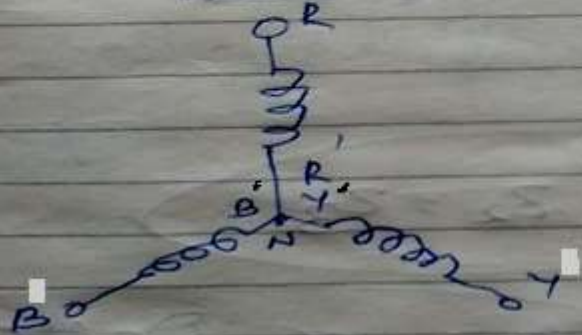


Three phase four wire star connection

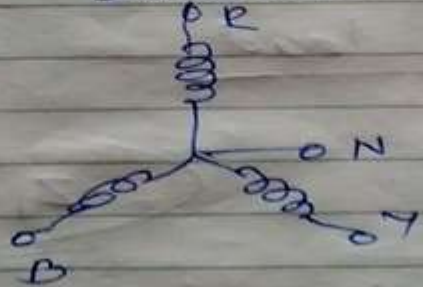


Three phase three wire delta connection




→ Star Connection:-

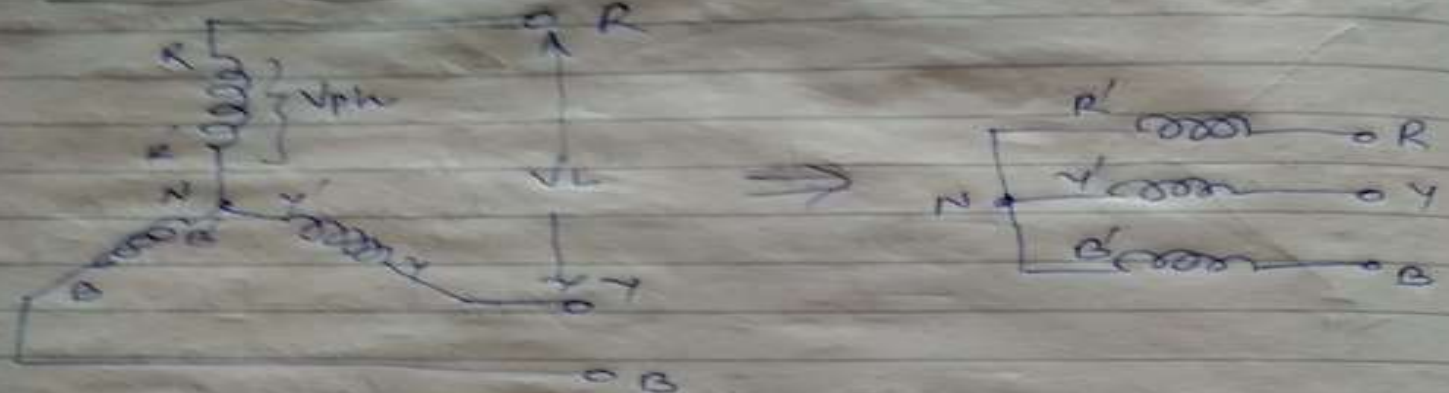

→ Delta Connection:-

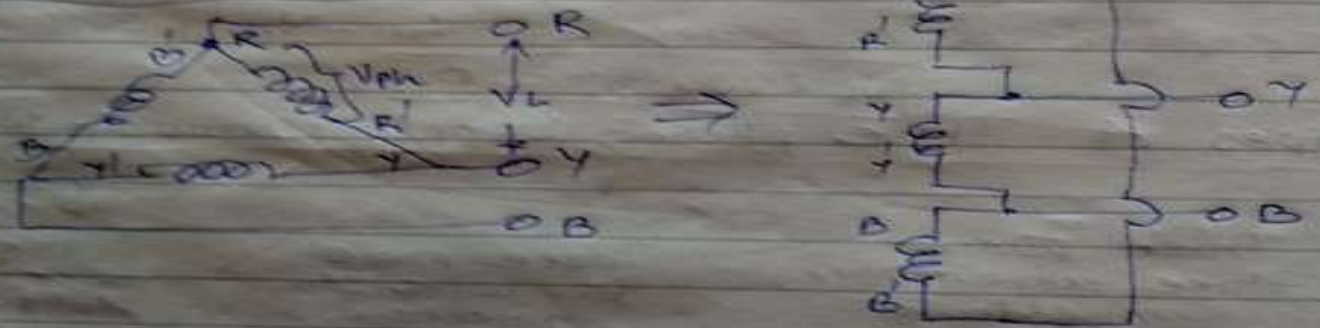


→ Balanced load

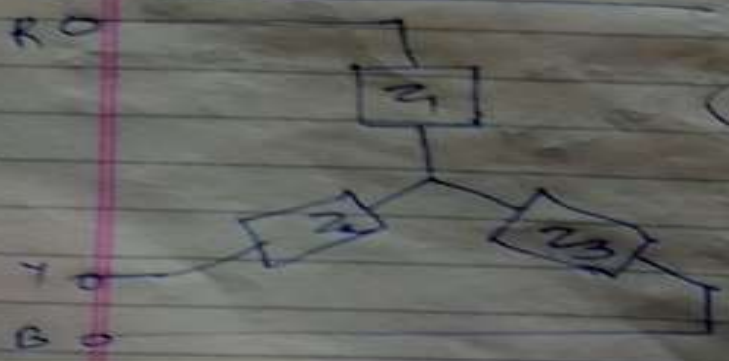

$Z_1 = Z_2 = Z_3$

Star or Delta

### Unbalanced Load :-

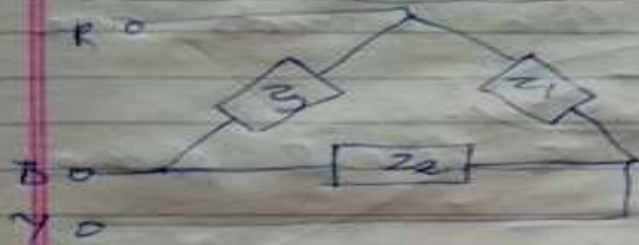


$$Z_1 \neq Z_2 \neq Z_3$$

Star or Delta

- 1) Phase Voltage  $\rightarrow V_{ph} \rightarrow$  Voltage <sup>across</sup> ~~between~~ phase (load)
- 2) Phase Current  $\rightarrow I_{ph} \rightarrow$  Current through phase (windings)
- 3) Line Voltage  $\rightarrow V_L \rightarrow$  Voltage across line (phases)
- 4) Line Current  $\rightarrow I_L \rightarrow$  Current through line (phase)
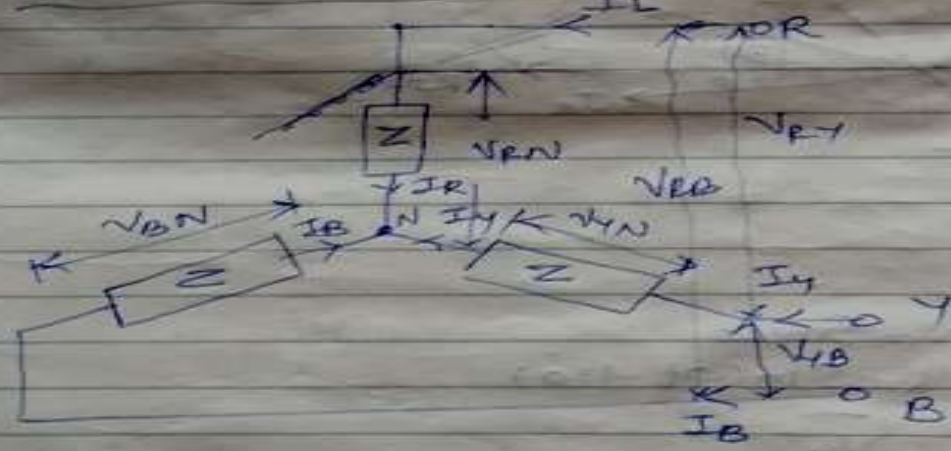
### \* Voltage & Current Relations in Star Connection



Here In 3-phase balanced load star connection  
 Phase Voltages -  $V_{ph} \rightarrow V_{rn}, V_{yn}, V_{bn}$   
 Line Voltages -  $V_L \rightarrow V_{rb}, V_{yb}, V_{br}$   
 Phase Currents  $\rightarrow I_{ph} \rightarrow I_R, I_Y, I_B$   
 Line Currents -  $I_L \rightarrow I_R, I_Y, I_B$


So, In 3-phase star connection with balanced load, Phase Currents & Line Currents are equal. So,  $I_L = I_{ph}$ .

Now, for getting relations of line & phase voltage,

Now, 
$$\vec{V}_{RY} = \vec{V}_{RN} + \vec{V}_{NY}$$

But 
$$\vec{V}_{NY} = -\vec{V}_{YN}$$
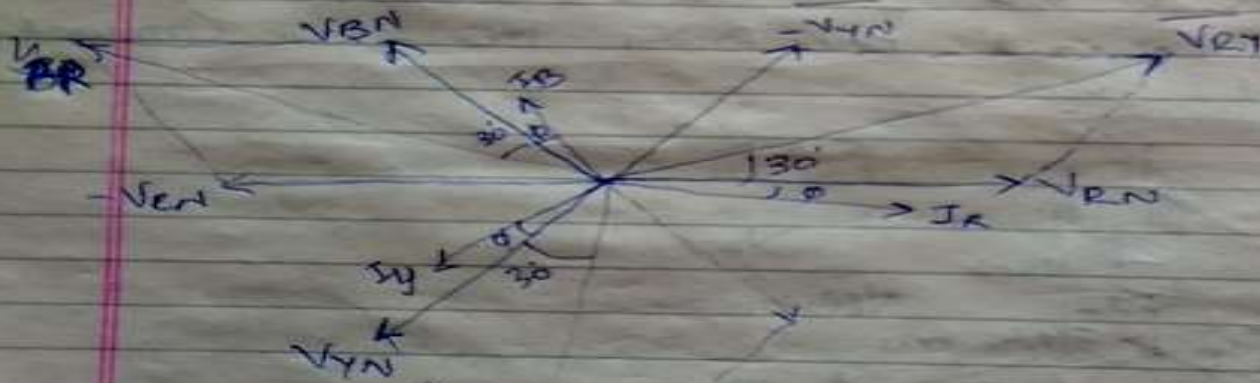
$$\therefore \vec{V}_{RY} = \vec{V}_{RN} - \vec{V}_{YN}$$



Let 
$$V_R = V_m \sin \omega t$$
  

$$V_Y = V_m \sin(\omega t - 120^\circ)$$

$$V_{RY} = V_R - V_Y$$

$$= V_m (\cos 0^\circ + j V_m \sin 0^\circ) - (V_m (\cos 120^\circ + j V_m \sin 120^\circ))$$
  

$$= V_m + j0 - (-0.5 V_m - j0.866 V_m)$$

$$\vec{V}_{RY} = V_m + 0.5 V_m + j0.866 V_m$$


$$\begin{aligned} \therefore V_{01} &= \sqrt{(1.5V_m)^2 + (0.866V_m)^2} \quad \angle -\tan^{-1}\left(\frac{0.866}{1.5}\right) \\ &= \sqrt{3} V_m \quad \angle 30^\circ \\ \uparrow \quad \left. \begin{array}{l} V_L = \sqrt{3} V_{ph} \end{array} \right\} \quad \angle 30^\circ \end{aligned}$$

$$\begin{aligned} \text{Total Power } P_T &= 3 P_{ph} \\ &= 3 \times V_{ph} \times I_{ph} \cos \phi \\ &= 3 \times \frac{1}{\sqrt{3}} V_L \times I_L \times \cos \phi \end{aligned}$$


$$\boxed{P_T = \sqrt{3} V_L I_L \cos \phi}$$

$$\text{Apparent Power (S)} = \sqrt{3} V_L I_L$$
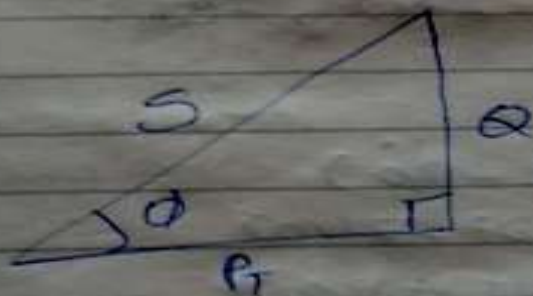
$$\text{Reactive Power (Q)} = \sqrt{3} V_L I_L \sin \phi$$



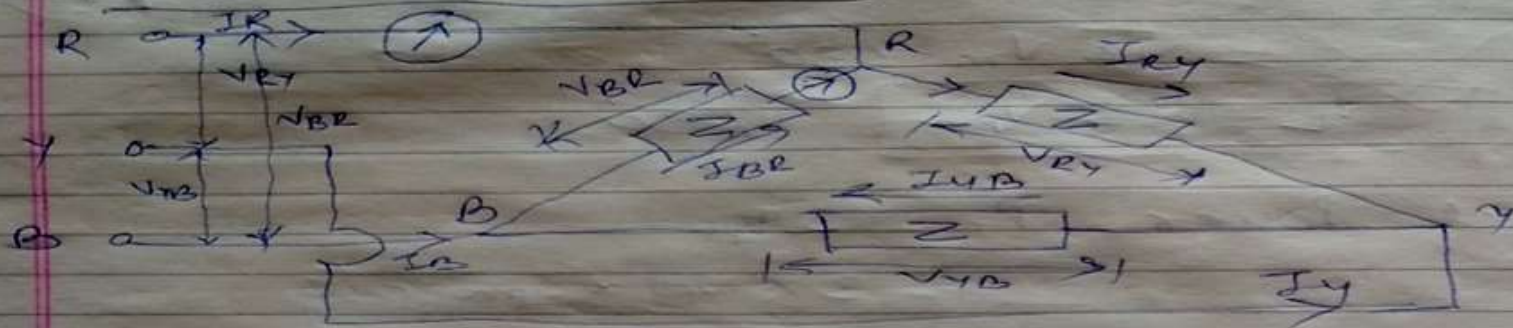\* Voltage & Current Relations in Balanced Load delta Connection:



Here Line Voltage  $V_L = V_{RT}, V_{BR}, V_{YB}$   
 Phase Voltage  $V_{ph} = V_{RT}, V_{YB}, V_{BR}$ .

So,  $V_L = V_{ph}$

Line Current =  $I_R, I_Y, I_B$ .

Phase Current =  $I_{RT}, I_{YB}, I_{BR}$ .

Here  $I_{RT} = I_m \sin \omega t$

$$I_{YB} = I_m \sin (\omega t - 120^\circ)$$

$$I_{BR} = I_m \sin (\omega t - 240^\circ) \\ = I_m \sin (\omega t + 120^\circ)$$

Applying KCL,


$$\bar{I}_Y + \bar{I}_{RT} = \bar{I}_{YB}$$

$$\bar{I}_R + \bar{I}_{BR} = \bar{I}_{RY}$$

$$\bar{I}_B + \bar{I}_{YB} = \bar{I}_{BR}$$
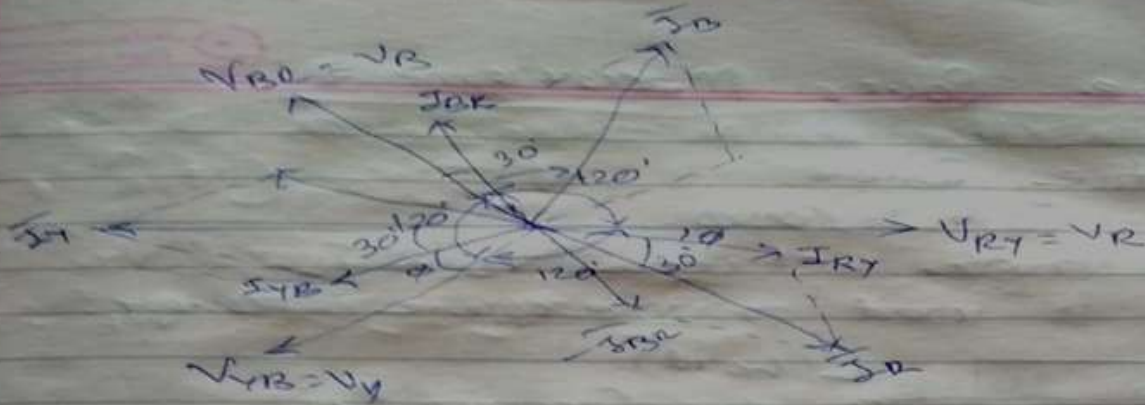
$$\therefore \bar{I}_R = \bar{I}_{RY} - \bar{I}_{BR}$$






$$\begin{aligned}
 \therefore I_R &= I_m \sin \omega t - I_m \sin(\omega t + 120^\circ) \\
 &= I_m \cos 0 + j I_m \sin 0 - I_m \cos 120^\circ - j I_m \sin 120^\circ \\
 &= I_m + 0 + 0.5 I_m - j 0.866 I_m \\
 I_R &= 1.5 I_m - j 0.866 I_m \\
 \therefore I_R &= \sqrt{(1.5 I_m)^2 + (-0.866 I_m)^2} \quad \angle -\tan^{-1} \left( \frac{-0.866}{1.5} \right) \\
 &= \sqrt{3} I_m \quad \angle -30^\circ \\
 I_R &= \sqrt{3} I_m \\
 \boxed{I_L = \sqrt{3} I_{ph} \quad \angle -30^\circ}
 \end{aligned}$$

$$\begin{aligned}
 P_T &= 3 V_{ph} I_{ph} \cos \phi \\
 &= 3 \times V_L \times \frac{I_L}{\sqrt{3}} \cos \phi
 \end{aligned}$$

$$\boxed{P_T = \sqrt{3} V_L I_L \cos \phi}$$
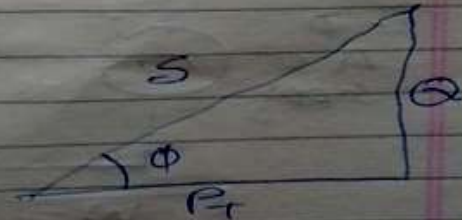
$$\begin{aligned}
 S &= V_{ph} I_{ph} = \sqrt{3} V_L I_L \\
 Q &= V_{ph} I_{ph} \sin \phi = \sqrt{3} V_L I_L \sin \phi
 \end{aligned}$$



## \* Three Phase Power Measurement :-

Total active Power

$$P_T = \sqrt{3} V_L I_L \cos \phi$$

$\phi$  is the angle between  $V_L$  &  $I_L$

Wattmeter is used to measure power




→ Current coil is between M and L it is connected in series. Resistance is small.

→ Voltage coil (Pressure coil) is between C and L. It is connected across the supply to measure voltage. Resistance is large.

$$W = V_{pc} \times I_c \times \cos \phi$$

$\downarrow$                        $\downarrow$                        $\downarrow$                        $\downarrow$   
 Wattmeter reading    Voltage across voltage coil    Current through current coil    Angle between  $V_{pc}$  and  $I_c$

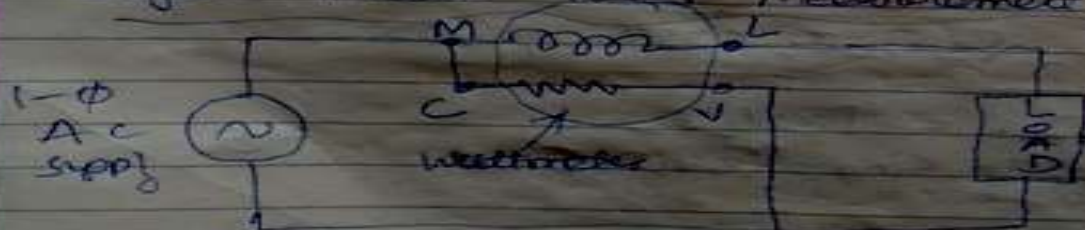→ Single phase Power measurement using a Wattmeter :-



$$W = V_{ph} I_{ph} \cos \phi$$

# \* Power Measurement in 3- $\phi$ AC Circuits


There are main three methods

- 1) One wattmeter method
- 2) Two wattmeter method
- 3) Three wattmeter method

## \* Two Wattmeter method for Star Connection

Balanced load:


Circuit Diagram:-

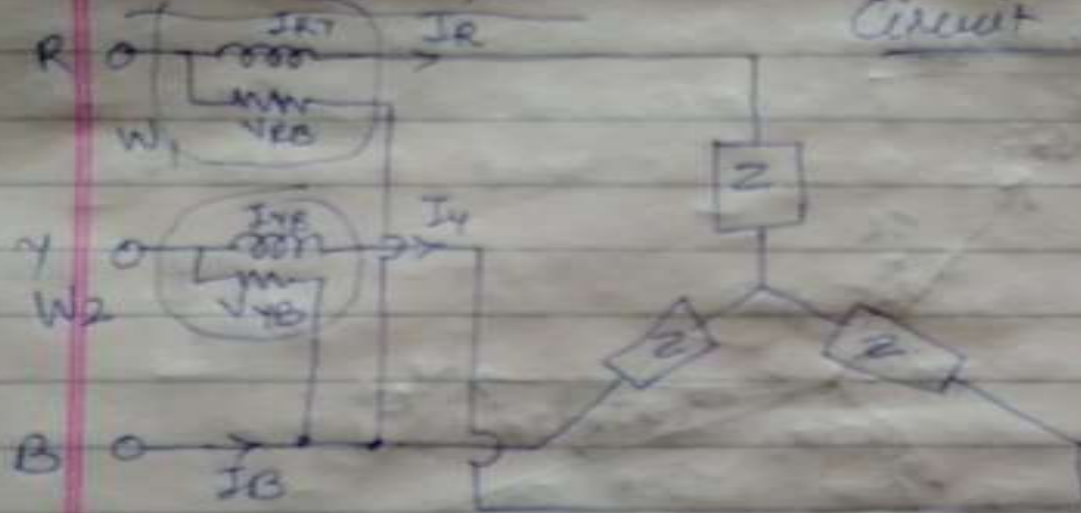

Now from wattmeter  $W_1 = V_{AB} I_A \cos(\hat{V}_{AB} \hat{I}_A)$   
 $= V_L I_L \cos(\hat{V}_{AB} \hat{I}_A)$

& for wattmeter  $W_2 = V_{CB} I_C \cos(\hat{V}_{CB} \hat{I}_C)$   
 $W_2 = V_L I_L \cos(\hat{V}_{CB} \hat{I}_C)$

Phasor Diagram -

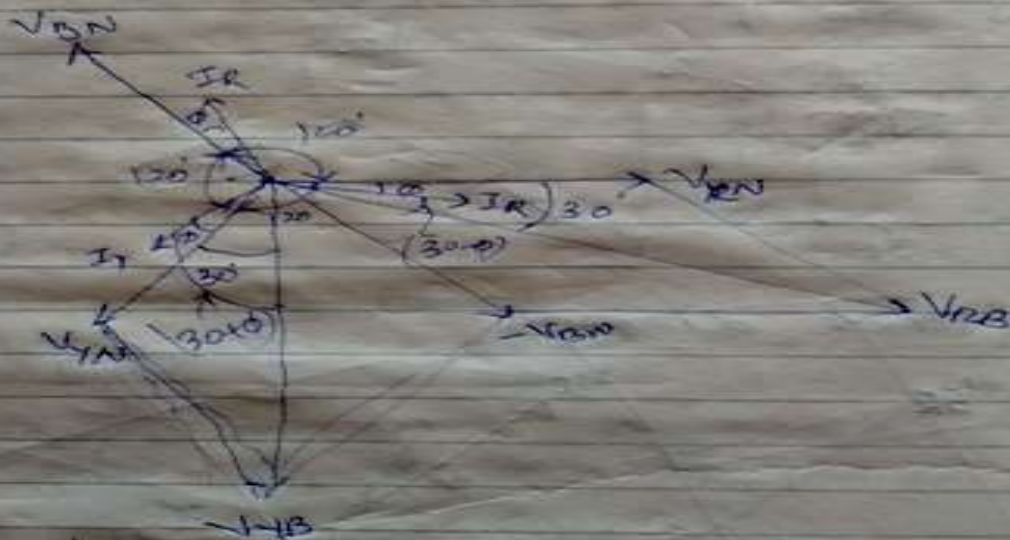

from the phasor diagram

$$W_1 = V_L I_L \cos(30 - \phi)$$

$$W_2 = V_L I_L \cos(30 + \phi)$$

Now, total active power

$$W = W_1 + W_2$$

$$= V_L I_L \cos(30 - \phi) + V_L I_L \cos(30 + \phi)$$

$$= V_L I_L [\cos(30 - \phi) + \cos(30 + \phi)]$$

$$= V_L I_L [\cos 30 \cos \phi + \sin 30 \sin \phi + \cos 30 \cos \phi - \sin 30 \sin \phi]$$

$$= \sqrt{3} I_L [2 \cos 30^\circ \cos \phi]$$

$$= \sqrt{3} I_L \left[ 2 \times \frac{\sqrt{3}}{2} \times \cos \phi \right]$$


$$W = \sqrt{3} \sqrt{3} I_L \cos \phi$$

$$\therefore W = W_1 + W_2 = \sqrt{3} \sqrt{3} I_L \cos \phi$$

\* Two Wattmeter method for Delta Connection  
Balanced load =



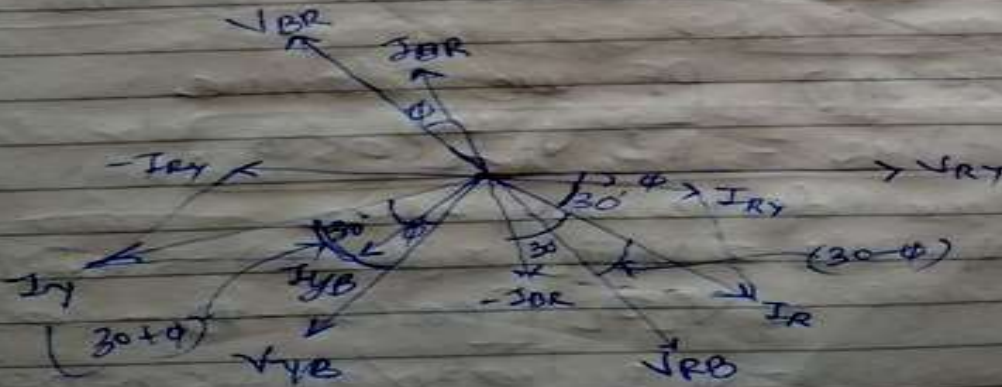for Wattmeter  $W_1 = V_{RB} I_R \cos(\angle V_{RY} I_R)$   
Wattmeter  $W_2 = V_{YB} I_Y \cos(\angle V_{YB} I_Y)$ .



from phasor diagram

$$W_1 = V_{RB} I_R \cos(30 - \phi)$$

$$W_1 = V_L I_L \cos(30 - \phi)$$

$$\& W_2 = V_{YB} I_Y \cos(30 + \phi)$$

$$W_2 = V_L I_L \cos(30 + \phi)$$

So, total Active Power

$$W = W_1 + W_2 = V_L I_L \cos(30 - \phi) + V_L I_L \cos(30 + \phi)$$

$$= V_L I_L [\cos(30 - \phi) + \cos(30 + \phi)]$$

$$= V_L I_L [\cos 30 \cos \phi + \sin 30 \sin \phi + \cos 30 \cos \phi - \sin 30 \sin \phi]$$

$$= V_L I_L [2 \cos 30 \cos \phi]$$

$$= V_L I_L \left[ 2 \times \frac{\sqrt{3}}{2} \times \cos \phi \right]$$

$$\boxed{W = W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi}$$

\* Power factor Measurement by two wattmeter  
meter method :-

For ~~correcting~~ PF we derive

$$\boxed{W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi}$$

Now, we derive  $W_1 - W_2$

$$\therefore W_1 - W_2 = V_L I_L \cos(30 - \phi) - V_L I_L \cos(30 + \phi)$$

$$= V_L I_L [\cos(30 - \phi) - \cos(30 + \phi)]$$

$$= V_L I_L [\cos 30 \cos \phi + \sin 30 \sin \phi - \cos 30 \cos \phi + \sin 30 \sin \phi]$$

$$= \sqrt{3} I_L [2 \sin 30 \cos \phi]$$

$$= \sqrt{3} I_L [2 \times \frac{1}{2} \times \cos \phi]$$

$$\boxed{W_1 - W_2 = \sqrt{3} I_L \sin \phi}$$

$$\text{And } \frac{W_1 - W_2}{W_1 + W_2} = \frac{\sqrt{3} I_L \sin \phi}{\sqrt{3} I_L \cos \phi}$$

$$\frac{W_1 - W_2}{W_1 + W_2} = \frac{1}{\sqrt{3}} \tan \phi$$

$$\therefore \tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)}$$

$$\therefore \phi = \tan^{-1} \left[ \frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)} \right]$$

$$\therefore \text{Power factor } \cos \phi = \cos \left[ \tan^{-1} \left( \frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)} \right) \right]$$

$$\text{if } \phi = 0, \quad W_1 = \sqrt{3} I_L \cos 30 = \frac{\sqrt{3}}{2} \sqrt{3} I_L$$

$$W_2 = \sqrt{3} I_L \cos 30 = \frac{\sqrt{3}}{2} \sqrt{3} I_L$$

$$\therefore W = 2W_1 = 2W_2$$

$$\text{if } \phi = 60, \quad W_1 = \sqrt{3} I_L \cos(-30) = \frac{\sqrt{3}}{2} \sqrt{3} I_L$$

$$W_2 = \sqrt{3} I_L \cos 90 = 0$$

$$\therefore W = W_1$$

$$\text{if } \phi = 90$$

$$W_1 = \sqrt{3} I_L \cos(-60) = \frac{1}{2} \sqrt{3} I_L$$

$$W_2 = \sqrt{3} I_L \cos(30) = \frac{1}{2} \sqrt{3} I_L$$

$$\therefore W = W_1 = W_2$$

Reactive Power  $Q = \sqrt{3} V_L I_L \sin \phi$

$$Q = \sqrt{3} (W_1 - W_2)$$

\* Merits (Advantages) of two wattmeter method:-

- 1) We can use it for the balanced as well as unbalanced load.
- 2) For Star connection, No neutral point is required.
- 3) The Delta load need not be open to connect the wattmeter.
- 4) For balanced load it is possible to measure the power factor along with power.
- 5) We need to use only two wattmeters to measure power in three phase system.
- 6) It is possible to measure the reactive power for the balanced load.

\* Demerits (Disadvantages):-

- 1) The polarity of  $W_1$  and  $W_2$  depends on the power factor so unless we identify them correctly they can lead us to wrong result.
- 2) This method is not used for three phase four wire system.