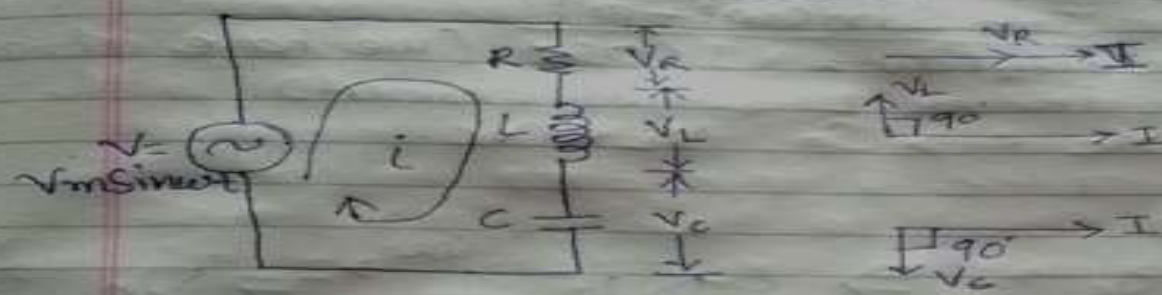


CHAPTER-2

AC CIRCUITS


* R-L-C Series Circuit :



→ In R-L-C Series circuit there are three possibilities.

- 1) $X_L > X_C$ → Behaved as an Inductive ckt.
- 2) $X_L < X_C$ → Behaved as a R-C ckt.
- 3) $X_L = X_C$ → Behaved as Resistive circuit.

1) $X_L > X_C$ → So $V_L > V_C$.

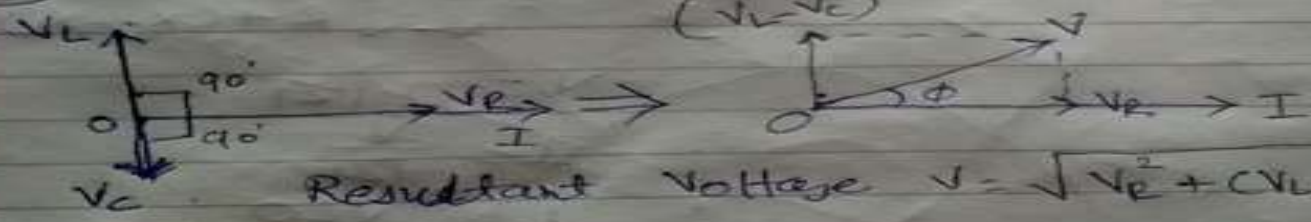

Resultant Voltage $V = \sqrt{V_R^2 + (V_L - V_C)^2}$

$$= \sqrt{(IR)^2 + (I(X_L - X_C))^2}$$

$$= I \sqrt{R^2 + (X_L - X_C)^2}$$

$$V = I |Z|$$

$$\therefore I = \frac{V}{|Z|}$$


$$I = \frac{V \cos \phi}{Z \cos \phi}$$

$$\therefore i = I_m \angle -\phi$$

$$\therefore \boxed{i = I_m \sin(\omega t - \phi)}$$

and Power Avg. $P_{av} = VI \cos \phi$ (We have already derived in R-L series circuit).

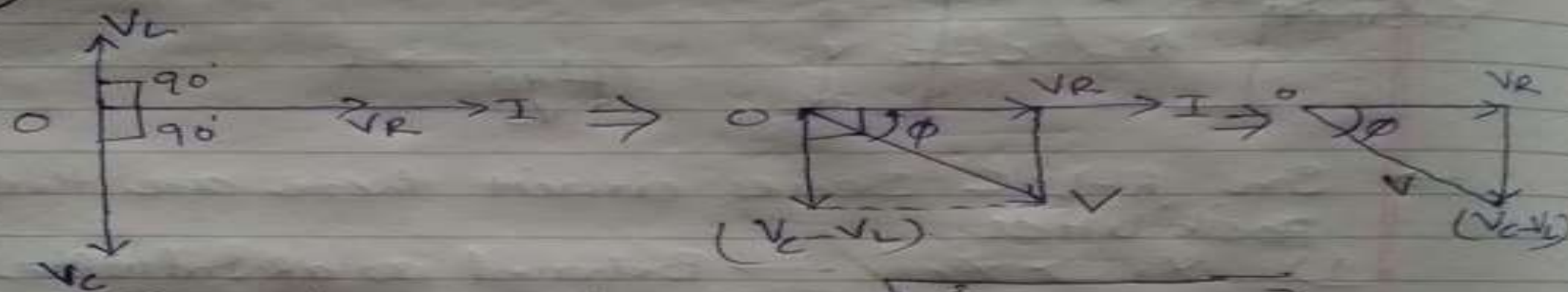e) $X_L < X_C \rightarrow$ So, $V_L < V_C$.



$$\begin{aligned} \text{Resultant Voltage } V &= \sqrt{V_R^2 + (V_C - V_L)^2} \\ &= \sqrt{(IR)^2 + (I(X_C - X_L))^2} \\ &= I \sqrt{R^2 + (X_C - X_L)^2} \end{aligned}$$

$$V = I |Z|$$

$$\therefore I = \frac{V}{|Z|}$$


$$\therefore i = \frac{V \angle 0}{Z \angle -\phi} = I_m \angle +\phi$$

$$\boxed{i = I_m \sin(\omega t + \phi)}$$


and Power Avg. $P_{av} = VI \cos \phi$ (We have already derived in R-C series ckt.)

3) $X_L = X_C \rightarrow$ So, $V_L = V_C$. So, R-L-C series circuit behaves as resistive circuit and it is known as R-L-C resonance circuit.

* Resonance in R-L-C Series Circuit:

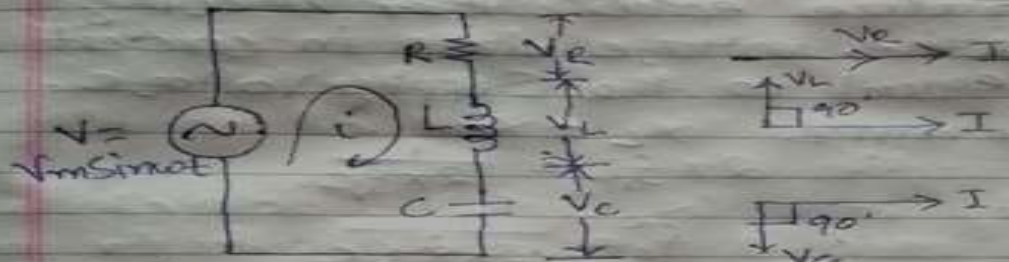

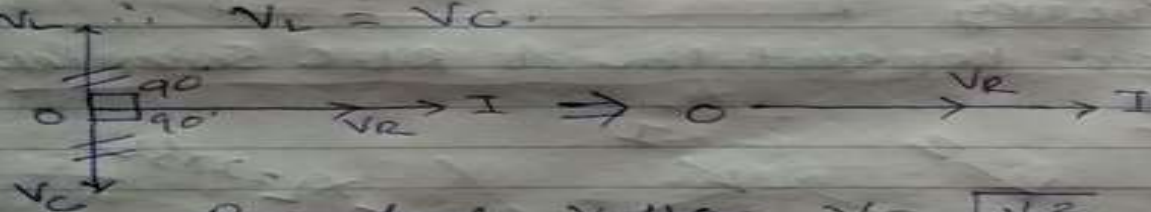\rightarrow In Resonance R-L-C series circuit
 $X_L = X_C$
 $V_L = V_C$



Resultant Voltage $V = \sqrt{V_R^2} = V_R$
 $V = IZ$

$$\therefore Z = \frac{V}{I} = R$$

\rightarrow So, In Resonance R-L-C series circuit the Impedance is purely resistive and minimum. Here the Current is maximum and such circuit is known as Resonance circuit and frequency is known as Resonance frequency.

→ Resonance circuit is also known as Acceptor circuit. It is used as tuning circuit in Radio.

→ In Resonance circuit $V_L = V_C$, so both voltage neutralize each other leaving behind a relative voltage drop in circuit which to be equal to the supply voltage


→ In Resonance $X_L = X_C$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}}$$

Resonant frequency $\rightarrow f_r = \frac{1}{2\pi\sqrt{LC}}$

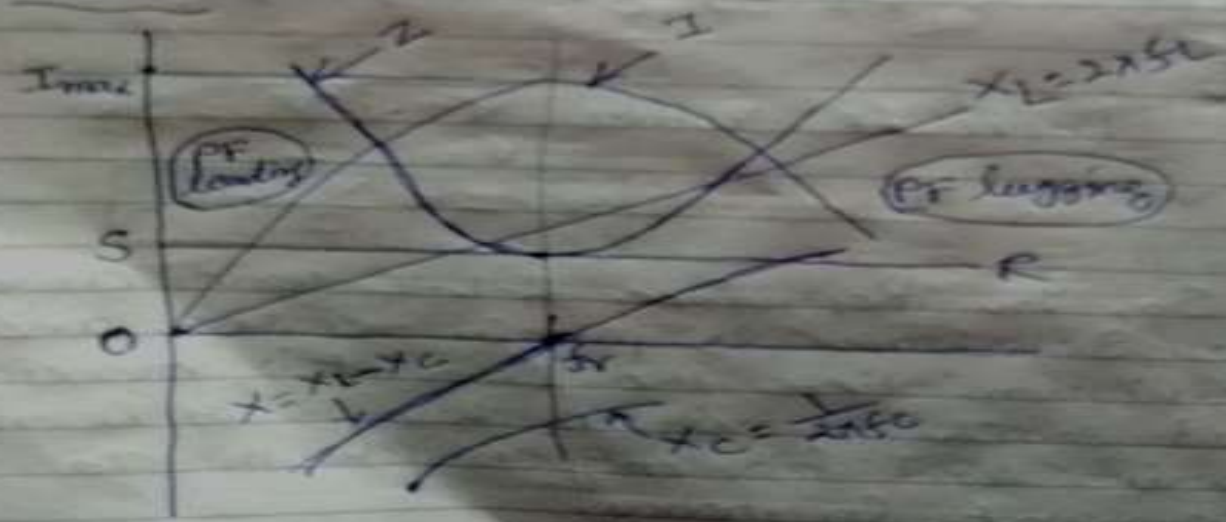* Graphical Representation of RLC Series Resonance Circuit:



→ The behaviour of R-L-C Series circuit in respect of Resonance as following.

- 1) As the frequency is changed, the value of Resistance R is independent of frequency. It doesn't vary with frequency as shown the horizontal line SR as shown in the graph.
- 2) X_L is directly proportional to the frequency and represented by $O-X_L$ in the graph.
- 3) X_C is inversely proportional to the frequency and shown in the graph.
- 4) Net reactive reactance $X = X_L - X_C$ is also shown and it is passed through the resonant frequency f_r .
- 5) Impedance Z is minimum and it is equal to R at resonant frequency and exponential to both the side as shown in the graph.
- 6) Current I is maximum at resonant frequency f_r and decreased on both the side of f_r .
- 7) When $f < f_r$, the power factor is leading because it behaves as capacitive circuit.
& when $f > f_r$, the power factor is lagging because it behaves as inductive circuit.

* Q-factor (Quality factor):-

→ At resonance $Z = R$ and therefore the current is maximum in the circuit and will cause large voltage drop across L and C and $V_L = V_C$ and opposition to the voltage drop across L and C. So, voltage drop occurred in Resistor R which is magnified the voltage. This voltage magnification is called Quality factor (Q-factor).

→ So, Quality factor (Q-factor) is defined as the ratio of potential drop across inductor or capacitor and the potential drop across the resistor.

∴ Q-factor = $\frac{\text{Potential drop across Inductor/Capacitor}}{\text{Potential drop across Resistor}}$

$$= \frac{X_L}{Y_R}$$

$$= \frac{2\pi fL}{R} = \frac{\omega_r L}{R} \left(f_r = \frac{1}{2\pi\sqrt{LC}} \right)$$

$$Q\text{-factor} = \frac{2\pi fL}{R \times 2\pi \times \sqrt{LC}} = \frac{1}{R} \times \frac{L}{\sqrt{LC}}$$

$$\boxed{Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}}$$

→ Q-factor of a series circuit indicates how many times the potential drop L and C is greater than apply voltage.

e.g. $V = 250V \rightarrow Q\text{-factor} = 20 \rightarrow V_L = V_C = 5000V$

1) A.C. Parallel Circuit :-



$$I = I_1 + I_2 + I_3 \quad \text{--- (1)}$$

$$\frac{V}{Z} = \frac{V}{Z_1} + \frac{V}{Z_2} + \frac{V}{Z_3}$$

$$\therefore \frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\therefore Y = Y_1 + Y_2 + Y_3 \quad \text{--- (2)}$$

Here $Y =$ admittance. (Unit is Siemens).

Eq. (1) can write

$$VY = VY_1 + VY_2 + VY_3$$

$$\therefore Y = Y_1 + Y_2 + Y_3 \quad \text{--- (3)}$$

Eq. (2) & (3) both are same.

Conductance :- (G)

$$Z = R + jX$$

$$\text{So, } Y = \frac{1}{R + jX}$$

$$\therefore Y = \frac{R - jX}{R + jX} \times \frac{1}{(R - jX)}$$

$$= \frac{(R - jX)}{(R^2 + X^2)}$$

$$Y = \frac{R}{R^2 + X^2} + \frac{jX}{R^2 + X^2}$$

$$Y = \frac{R}{Z^2} + \frac{jX}{Z^2}$$

$$\therefore Y = G + jB \Rightarrow |Y| = \sqrt{G^2 + B^2}, \phi = \tan^{-1}\left(\frac{B}{G}\right)$$



Here $G = \frac{R}{Z^2} = \text{Conductance}$ (Unit is Siemens)

Susceptance (B) :

$$B = \frac{X}{Z^2} = \text{Susceptance (Unit is Siemens)}$$

Polaris	+	-
Resistance, X	Inductive	Capacitive
Susceptance, B	Capacitive	Inductive

* Admittance Triangle :-

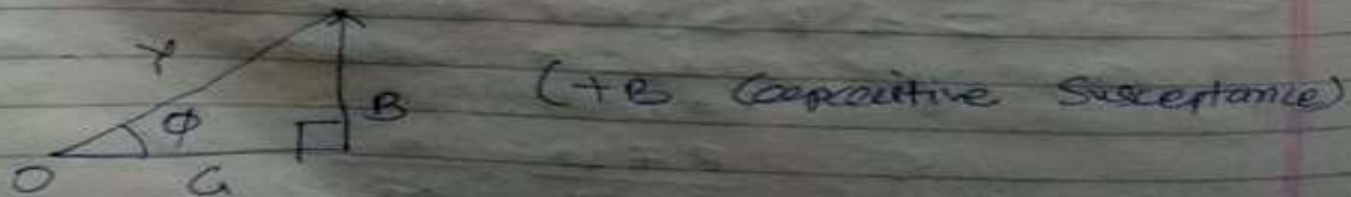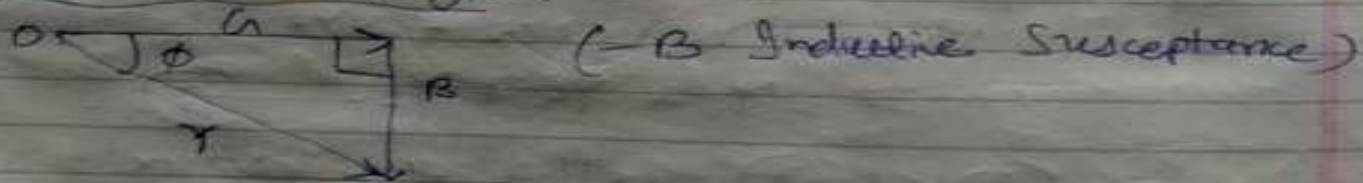

* Types of Parallel AC Circuits :-

- 1) Resistance in parallel with pure Inductor (R-L parallel)
- 2) Resistance in parallel with pure Capacitor (R-C parallel)
- 3) Series combination of R and L in parallel with a Capacitor in parallel (RL series & C in parallel).

→ 1) Resistance in parallel with Pure Inductor (R-L parallel)



Phasor diagram :-



$$I = I_R + I_L$$

$$I = \frac{V}{R} + \frac{V}{X_L}$$

Impedance :- Here $Z_1 = R + j0 = R \angle 0^\circ \Omega$

$$Z_2 = \textcircled{\ominus} + jX_L = X_L \angle 90^\circ \Omega$$

$$Z = Z_1 \parallel Z_2$$

$$= \frac{Z_1 \times Z_2}{Z_1 + Z_2}$$

$$= \frac{R \angle 0^\circ \times X_L \angle 90^\circ}{R + j0 + 0 + jX_L}$$

$$= \frac{R X_L \angle 90^\circ}{R + jX_L}$$

$$= \frac{R X_L \angle 90^\circ}{R + jX_L}$$

$$Z = \frac{R + jX_L \angle 90^\circ}{\sqrt{R^2 + X_L^2} \angle \tan^{-1}\left(\frac{X_L}{R}\right)}$$


$$\therefore Z = \frac{R + jX_L}{|Z_S|} \angle (90^\circ - \phi_S)$$

where $|Z_S| = \sqrt{R^2 + X_L^2}$ & $\phi = \tan^{-1}\left(\frac{X_L}{R}\right)$

Voltage & Current waveforms:

Here $V = V_m \sin \omega t$

& we get $i = I_m \sin(\omega t - \phi)$

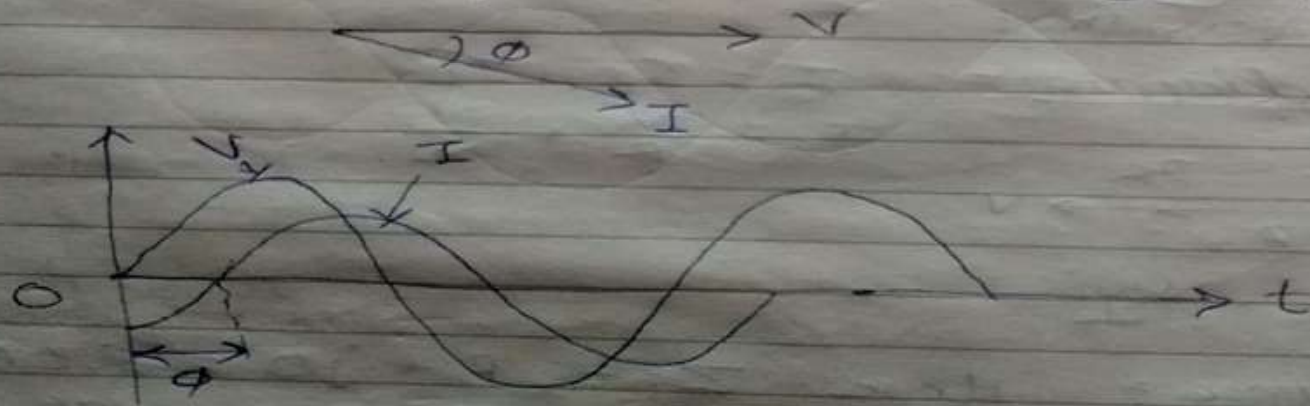


Power factor:

$$P.F. = \cos \phi$$

Here power factor is less than 1 by angle ϕ . Means current is lagging by angle ϕ to the voltage.

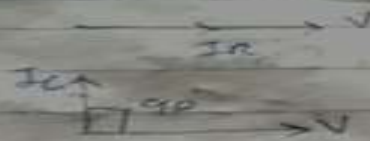→ 2) Resistance in parallel with pure Capacitor (RC parallel)



Phasor diagram -

$$I = I_R + I_C$$

$$I = \frac{V}{R} + \frac{V}{X_C}$$



Impedance - Here, $Z_1 = R + j0 = R \angle 0^\circ \Omega$
 $Z_2 = 0 - jX_C = X_C \angle -90^\circ \Omega$

$$\therefore Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$= \frac{R \angle 0^\circ \times X_C \angle -90^\circ}{R + j0 + 0 - jX_C}$$

$$= \frac{R X_C \angle -90^\circ}{R - jX_C}$$

$$Z = \frac{R X_C \angle -90^\circ}{\sqrt{R^2 + X_C^2} \angle \tan^{-1}\left(\frac{X_C}{R}\right)}$$

$$\therefore Z = \frac{R X_C}{|Z_S|} \angle (90^\circ + \phi)$$

Where $|Z_S| = \sqrt{R^2 + X_C^2}$ & $\phi = -\tan^{-1}\left(\frac{X_C}{R}\right)$

Voltage & Current Waveform:

Here $V = V_m \sin \omega t$
& we get $i = I_m \sin(\omega t + \phi)$.





Power factor:-

$$P.F. = \cos \phi$$

Here P.F. is leading because I leads voltage by an angle of ϕ .

Resonance in Parallel Circuit:-

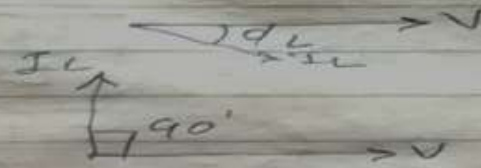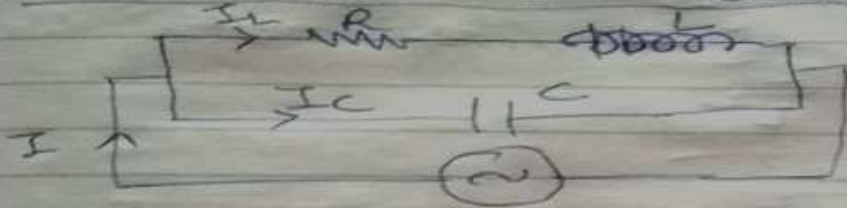

Phasor diagram:-



For Resonance, $I_C = I_L \sin \phi$.

$$I_C = \frac{V}{X_C}, \quad I_L = \frac{V}{Z_L}$$

$$Z_L = R + jX_L = \sqrt{R^2 + X_L^2}$$

$$\phi_L = \tan^{-1}\left(\frac{X_L}{R}\right)$$

$$\sin \phi_L = \frac{X_L}{Z_L}$$


$$\therefore \frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$

$$\therefore Z_L^2 = X_L \cdot X_C$$

$$\therefore R^2 + (\omega_0 L)^2 = \omega_0 L \times \frac{1}{\omega_0 C}$$

$$\therefore (\omega_0 L)^2 = \frac{L}{C} - R^2$$
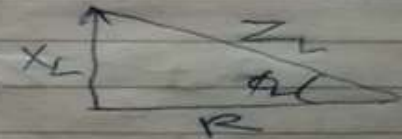
$$\therefore \omega_0^2 L^2 = \frac{L}{C} - R^2$$



$$\therefore \omega_r^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\therefore \omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\therefore 2\pi f_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\therefore f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad \leftarrow \text{Resonant frequency}$$

If R of the coil is negligible, so, $\frac{R^2}{L^2} \rightarrow 0$.

$$\therefore f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{1}{2\pi\sqrt{LC}}$$

→ To find the Dynamic Impedance,

$$I = I_L \cos \phi$$

$$\frac{V}{Z} = \frac{V}{Z_L} \cdot \frac{R}{Z_L}$$

$$\therefore \frac{1}{Z} = \frac{R}{Z_L^2}$$

But $Z_L^2 = X_L \cdot X_C = \frac{L}{C}$.

$$\therefore \frac{1}{Z} = \frac{RC}{L}$$

$$\therefore Z_D = \frac{L}{RC}$$




Parallel Resonance Ckt. is a Rejector Circuit




Resultant Current $I = \frac{V}{Z} = \frac{V}{4RC}$

→ In parallel resonance circuit I will be minimum because impedance is maximum.

$I = \frac{V}{Z}$ will be minimum

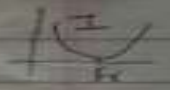

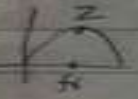Q-factor = $\frac{I_C}{I} = \frac{I_C \sin \phi}{I_L \cos \phi} = \tan \phi$
 $= \frac{X_L}{R} = \frac{2\pi f_r L}{R}$



* Comparison between Series & Parallel Resonance:

Sr. no.	Description	Series Resonance	Parallel Resonance
1.	f_r	$\frac{1}{2\pi \sqrt{LC}}$	$\frac{1}{2\pi \sqrt{LC}} = \frac{R^2}{L^2}$
2.	Impedance Z	Minimum	Maximum
3.	Z_{eff} (Effective Impedance)	R	$\frac{L}{CR}$
4.	Current	$\frac{V}{R}$	$\frac{V}{4RC}$
5.	Power factor	unity	unity
6.	Magnifies	Voltage	Current.
7.	Q-factor	$\frac{\omega_r L}{R}$	$\frac{\omega_r L}{R}$
8.	Application (used for)	Accepter	Rejector.