

Class notes : APE,


Prepared By: Dr. Shaikh Mohammed Suhel (Ph.D, M.Tech, Gate, B.E)

Associate Professor and Department Head


Multilevel Inverter

Definition: The number of steps in the voltage of the output terminal with respect to any arbitrary internal reference point.

 
- Generated stepped waveform output voltage with adjusted frequency and amplitude.



2 level Inverter

 

3 level Inverter

 

5 level Inverter

Question: Why Multilevel Inverter is required? Or Difference between two level and Multilevel Inverter

2 Level Inverter	Multilevel Inverter
1) The stress on the device is high in case of two level inverter as $\frac{dv}{dt}$ is high in this configuration.	1) The stress on the device is low as voltage increases in stepped manner and so that $\frac{dv}{dt}$ is lower in this type configuration
2) Higher voltage operation is difficult	2) Higher voltage operation is easily

- 3) Filter size requirement is higher in two level
- 4) As power level increases, dc link voltage and switching frequency has to be reduced. This action lead to generate lower order harmonics (7th and 9th)
- 5) Device rating is high in case of 2 level inverter

possible as voltage is distributed among the series connected switches

- 3) MLI (Multi level Inverter) reduces the filter size requirement
- 4) MLI reduces the lower order harmonics and operates with lower switching frequencies
- 5) Device rating reduces significantly and this will reduces the cost of MLI

Types of MLI:

- 1) Diode clamped MLI or Neutral Point Clamped (NPC) MLI
- 2) Flying capacitor type MLI
- 3) Cascade H-Bridge MLI

Diode Clamped MLI:

Three level Diode Clamped MLI:

- Fig. 1 shows the one leg of Inverter (total three legs of three phase)
- No of Capacitor require= $(N-1) = 2$; where N is the level of Inverter
- No of switches required/phase= $2(N-1) = 4$
- Any times switches 'ON'= $(N-1) = 2$


 



Fig.1: 3-Level Diode clamped MLI

When S1 and S2 are 'ON':

 


- Here, $V_{ax}=V_{dc}$ and $V_{ao}=V_{dc}/2$;
- The positive direction of current flows through $-C_2-C_1$ -switch S_1 and S_2
- The negative direction of current (Load to source) flows through diode D_1 and $D_2-C_1-C_2$

When S2 and S3 are 'ON':

 

- Here, $V_{ax}=V_{dc}/2$ and $V_{ao}=0$;
- The positive direction of current flows through $-D_A$ -switch S_2
- The negative direction of current (Load to source) flows through-switch S_3 -and D_A'

When S3 and S4 are 'ON':

 

- Here, $V_{ax}=0$ and $V_{ao}= -V_{dc}/2$;
- The positive direction of current flows through $-C_1-C_2$ -diode D_4 and D_3
- The negative direction of current (Load to source) flows through switch S_3-S_4 and $-C_2-C_1$

 



Fig.2: Output Pole Voltage V_{AO}

Switching state of 3 level Inverter:


Switching state	S_1	S_2	S_3	S_4	V_{AO}	V_{AX}
	ON	ON	OFF	OFF	$V_{dc}/2$	V_{dc}
	OFF	ON	ON	OFF	0	$V_{dc}/2$
	OFF	OFF	ON	ON	$-V_{dc}/2$	0

Four level Diode Clamped MLI:

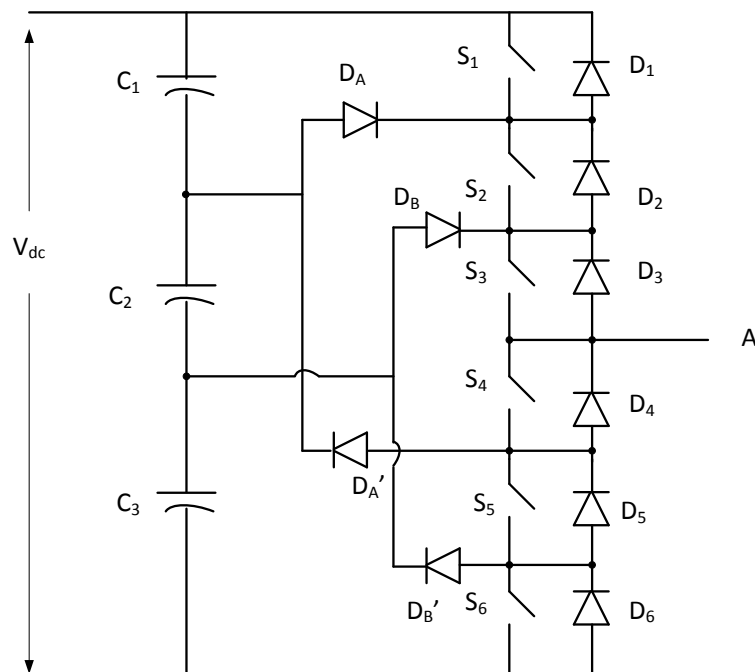- Fig. 4 shows the one leg of Inverter (total three legs of three phase)
- No of Capacitor require= $(N-1) = 3$; where $N (=4)$ is the level of Inverter
No of switches required/phase= $2(N-1) = 6$
Any times switches 'ON'= $(N-1) = 3$




When S_1, S_2 and S_3 are 'ON':

 


- Here, $V_{ax}=V_{dc}$;
- The positive direction of current flows through $C_3-C_2-C_1$ -switch $S_1 S_2$ and S_3
- The negative direction of current (Load to source) flows through diode $D_1 D_2$ and $D_3-C_1-C_2-C_3$

When S_2, S_3 and S_4 are 'ON':

 


- Here, $V_{ax}=2V_{dc}/3$;
- The positive direction of current flows through D_A -switch S_2 and S_3
- The negative direction of current (Load to source) flows through S_4 diode D_A'

When S_3, S_4 and S_5 are 'ON':

 

- Here, $V_{ax} = V_{dc}/3$;
- The positive direction of current flows through D_B –switch S_3
- The negative direction of current (Load to source) flows through S_4 S_5 diode D_B'

When S_4, S_5 and S_6 are 'ON':

 

- Here, $V_{ax} = 0$;

Features of NPC MLI (or Diode Clamped MLI):

- In 4 Level NPC MLI D_A has to block $1/3 V_{dc}$ (Rating)
- $D_{A'}$ has to block $2/3 V_{dc}$
- Separate heat sink required in this case
- Voltage unbalance issue: When o/p voltage is V_{dc} : C_1, C_2, C_3 supply the power and When o/p voltage is $2/3 V_{dc}$ C_2, C_3 supply the power-> so voltage across C_1 increases compare to other two capacitors.

 


Fig.4: Output Voltage V_{AX}

Advantages:

- Filter size reduces
- All switches operate at fundamental frequency so switching losses are reduced and efficiency increase.
- Control Method is simple

Disadvantage:

- When no of level increases, no of clamping diode increases.