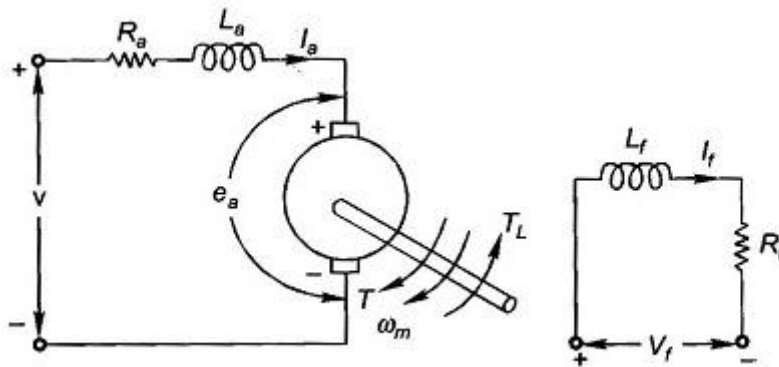


Lecture Note Electrical Drives

Prepared By: Dr. Shaikh Mohammed Suhel

Ph.D, GATE, M.Tech, B.E. Electrical

Q: Dynamic modelling of DC Machine



When supply V_a is given to stator winding, flux produced in stator winding linked to Rotor and Rotor starts rotating as a result back emf is generated. Applying KVL in armature circuit:

$$V_a = I_a R_a + L_a \frac{dI_a}{dt} + E_b \quad (1)$$

Where,

V_a is the armature voltage in volts.

I_a is the armature current in ampere.

L_a is the armature inductance in Henry.

R_a is the armature resistance in ohms.

E_b is the back emf in volts.

By applying laplace transformation to (1):

$$V_a(s) = I_a(s) R_a + s L_a I_a(s) + E_b(s)$$

$$I_a(s) = \frac{V_a(s) - E_b(s)}{R_a + s L_a} \quad (2)$$

Similarly for field winding if we apply KVL and transforming into laplace domain

$$I_f(s) = \frac{V_f(s)}{R_f + s L_f}$$

V_f is the Field Voltage in volts.

R_f is the field resistance in ohms.

I_f is the Field current in ampere.

Now back emf can be obtained as

$$\begin{aligned}
E_b &= \frac{ZP}{60A} \phi N \\
&= \frac{ZP}{60A} \phi \frac{60\omega}{2\pi} \\
&= \frac{ZP}{A} \phi \frac{\omega}{2\pi} \\
&= \frac{ZP}{2\pi A} \phi \omega \\
&= \frac{ZP}{2\pi A} K I_f \omega \\
&= K_b I_f \omega
\end{aligned}$$

Where,

Z is the number of conductors.

P is the number of poles.

A is the number of Parallel Path.

ϕ is the flux in weber.

N is the number of turns in rpm.

ω is the Speed in rad/sec.

Motor torque equation can be written as

$$\begin{aligned}
T &= K_t I_a \phi \\
&= \frac{ZP}{2\pi A} \phi I_a \\
&= K_t I_f I_a
\end{aligned}$$

Finally Speed of the machine can be obtained as:

$$T_e = T_L + J \frac{d\omega}{dt}$$

$$T_e(s) = T_L(s) + sJ\omega$$

$$\omega = \frac{T_e - T_L}{Js}$$

T_e is the motor Torque in N.m

T_L is Load Torque in N.m

J is the inertia.

