

# CHAPTER 13

## **ADC, DAC, AND SENSOR INTERFACING**

# ADC Devices


- ADCs (analog-to-digital converters) are among the most widely used devices for data acquisition
  - A physical quantity, like temperature, pressure, humidity, and velocity, etc., is converted to electrical (voltage, current) signals using a device called a transducer, or sensor
  - We need an analog-to-digital converter to translate the analog signals to digital numbers, so microcontroller can read them

# ADC804 Chip

- ADC804 IC is an analog-to-digital converter
  - It works with +5 volts and has a resolution of 8 bits
  - Conversion time is another major factor in judging an ADC
    - Conversion time is defined as the time it takes the ADC to convert the analog input to a digital (binary) number
    - In ADC804 conversion time varies depending on the clocking signals applied to CLK R and CLK IN pins, but it cannot be faster than 110  $\mu$ s

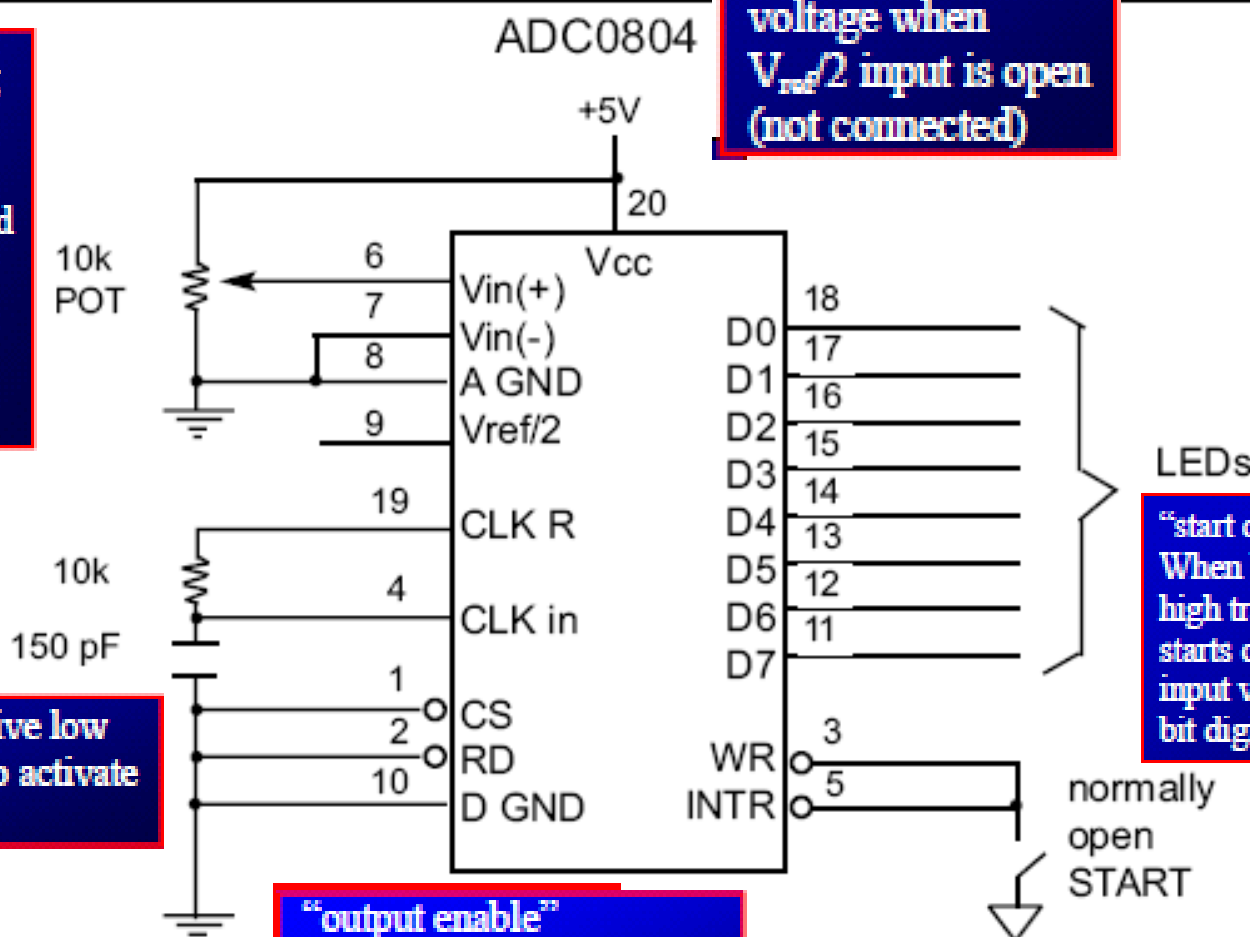**+5V power supply or a reference voltage when  $V_{ref}/2$  input is open (not connected)**

**Differential analog inputs where  $V_{in} = V_{in}(+) - V_{in}(-)$   
 $V_{in}(-)$  is connected to ground and  $V_{in}(+)$  is used as the analog input to be converted**



**CS is an active low input used to activate ADC804**

**“output enable”  
a high-to-low RD pulse is used to get the 8-bit converted data out of ADC804**

**“start conversion”  
When WR makes a low-to-high transition, ADC804 starts converting the analog input value of  $V_{in}$  to an 8-bit digital number**

Figure 13-1. ADC0804

(in free running mode)


# ADC804 Chip (cont.)

- CLK IN and CLK R
  - CLK IN is an input pin connected to an external clock source
  - To use the internal clock generator (also called self-clocking), CLK IN and CLK R pins are connected to a capacitor and a resistor, and the clock frequency is determined by

$$f = \frac{1}{1.1RC}$$

- Typical values are  $R = 10K$  ohms and  $C = 150$  pF
  - We get  $f = 606$  kHz and the conversion time is  $110$   $\mu$ s
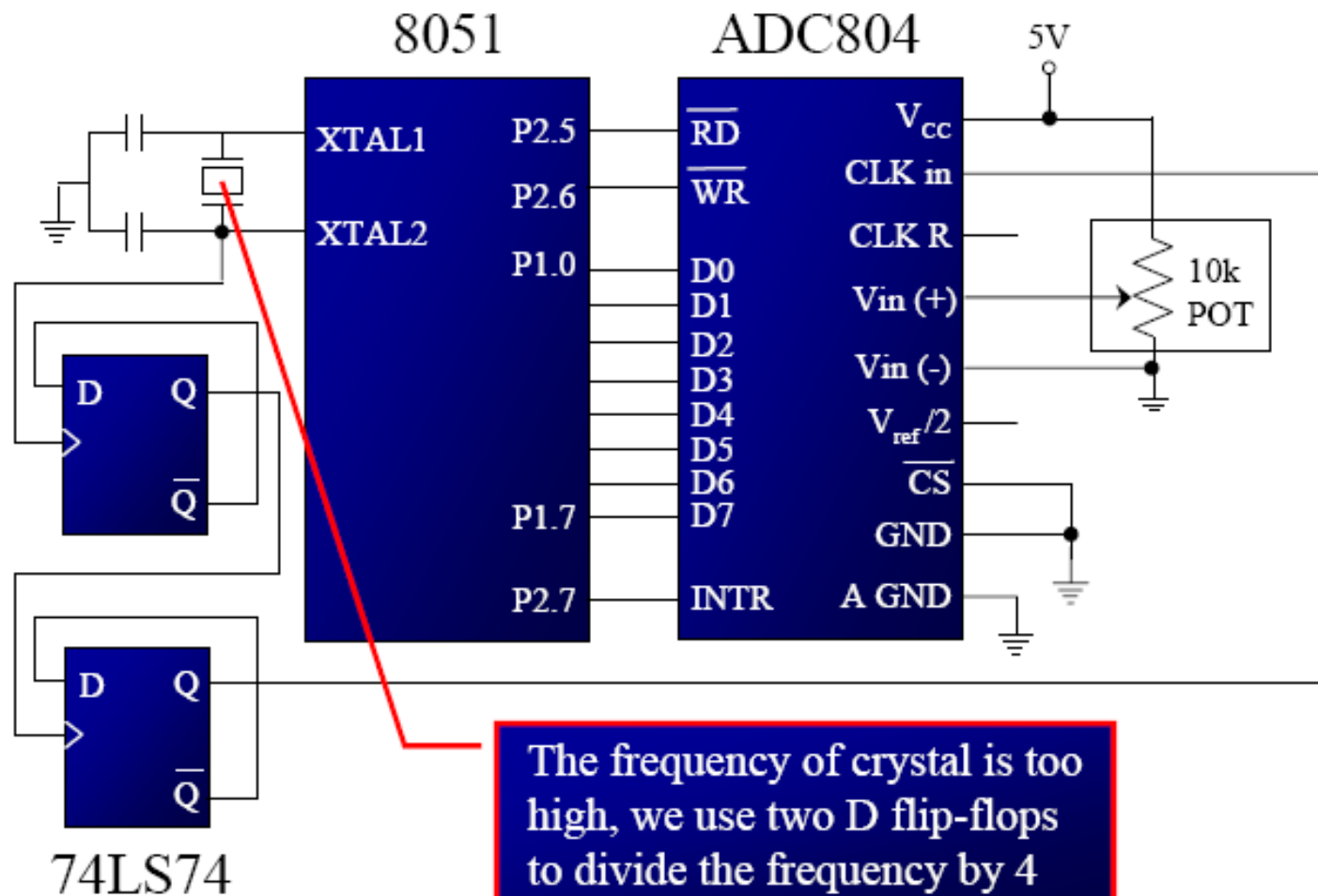
## 8051 Connection to ADC804 with Clock from XTAL2 of 8051



# ADC804 Chip (cont.)

- $V_{\text{ref}}/2$ 
  - It is used for the reference voltage
    - If this pin is open (not connected), the analog input voltage is in the range of 0 to 5 volts (the same as the  $V_{\text{cc}}$  pin)
    - If the analog input range needs to be 0 to 4 volts,  $V_{\text{ref}}/2$  is connected to 2 volts

## $V_{\text{ref}}/2$ Relation to $V_{\text{in}}$ Range

$V_{\text{ref}}/2(\text{v})$	$V_{\text{in}}(\text{V})$	Step Size ( mV)
Not connected*	0 to 5	$5/256=19.53$
2.0	0 to 4	$4/255=15.62$
1.5	0 to 3	$3/256=11.71$
1.28	0 to 2.56	$2.56/256=10$
1.0	0 to 2	$2/256=7.81$
0.5	0 to 1	$1/256=3.90$

Step size is the smallest change can be discerned by an ADC

# ADC804 Chip (cont.)

- D0-D7
  - The digital data output pins
    - These are tri-state buffered
      - The converted data is accessed only when CS = 0 and RD is forced low
    - To calculate the output voltage, use the following formula

$$D_{out} = \frac{V_{in}}{\text{step size}}$$

- $D_{out}$  = digital data output (in decimal),
- $V_{in}$  = analog voltage, and
- step size (resolution) is the smallest change




# ADC804 Chip (cont.)

- Analog ground and digital ground
  - Analog ground is connected to the ground of the analog  $V_{in}$ 
    - To isolate the analog  $V_{in}$  signal from transient voltages caused by digital switching of the output D0 – D7
    - This contributes to the accuracy of the digital data output
  - Digital ground is connected to the ground of the  $V_{cc}$  pin
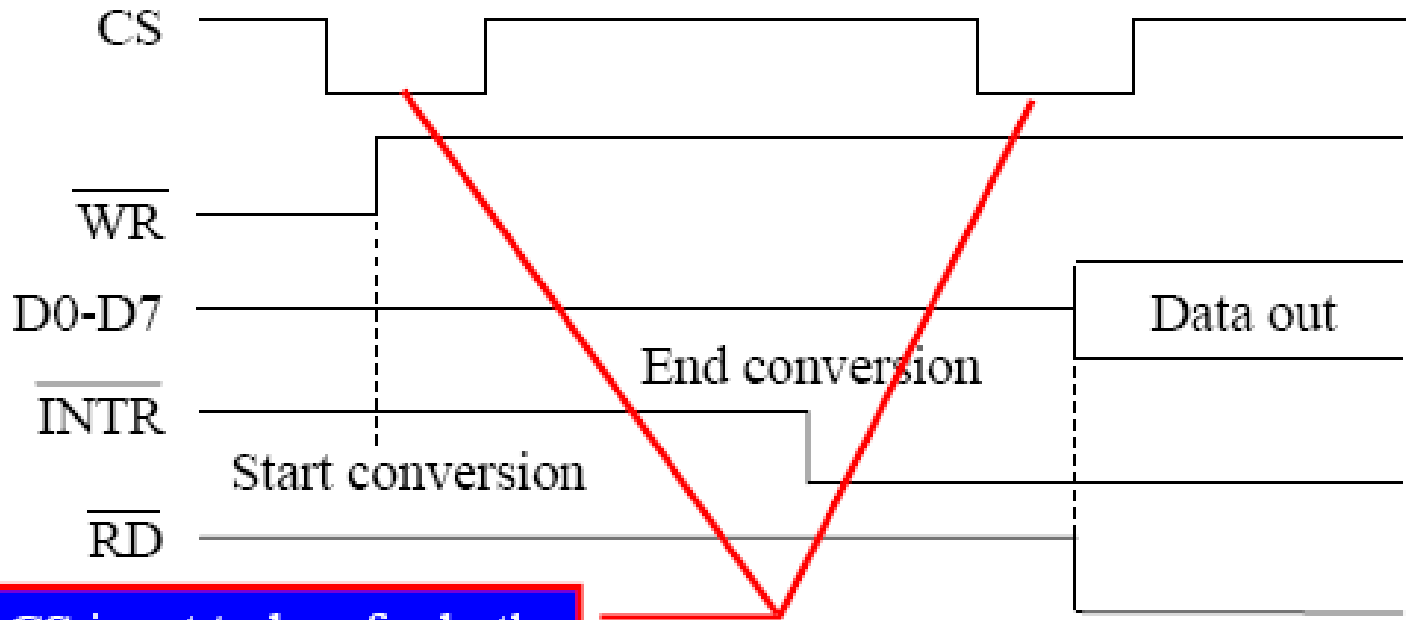
# ADC804 Chip (cont.)


- The following steps must be followed for data conversion by the ADC804 chip
  - Make CS = 0 and send a low-to-high pulse to pin WR to start conversion
  - Keep monitoring the INTR pin
    - If INTR is low, the conversion is finished
    - If the INTR is high, keep polling until it goes low
  - After the INTR has become low, we make CS = 0 and send a high-to-low pulse to the RD pin to get the data out of the ADC804



CS is set to low for both WR and RD pulses

Read it

## ADC804 Free Running Test Mode

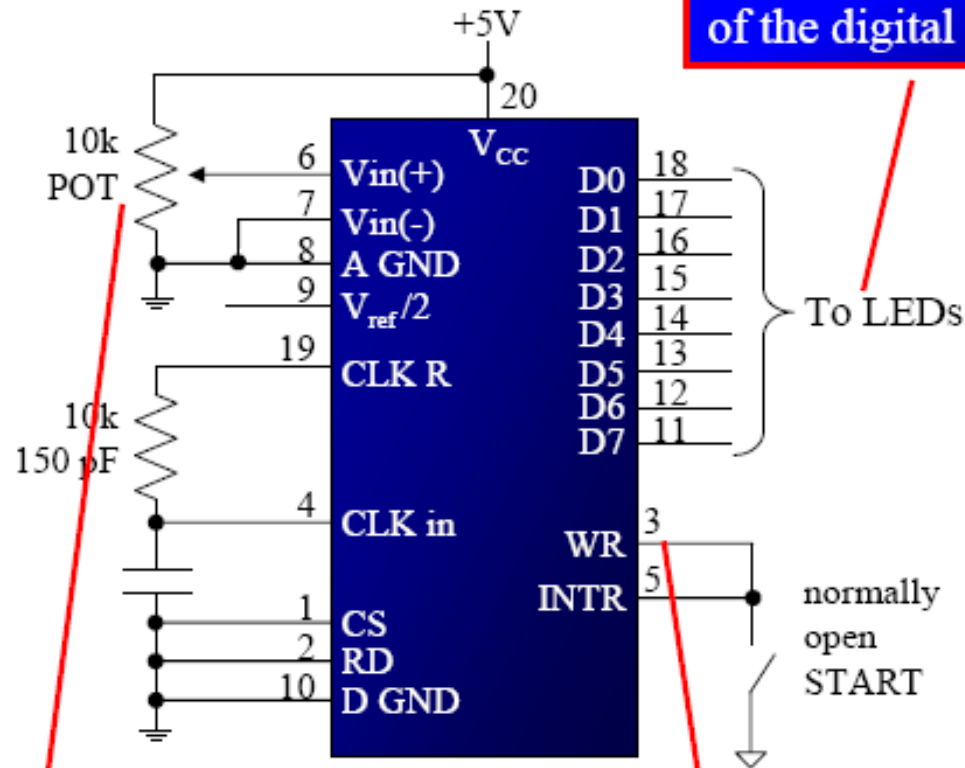


The binary outputs are monitored on the LED of the digital trainer

a potentiometer used to apply a 0-to-5 V analog voltage to input V<sub>in</sub> (+) of the 804 ADC

The CS input is grounded and the WR input is connected to the INTR output
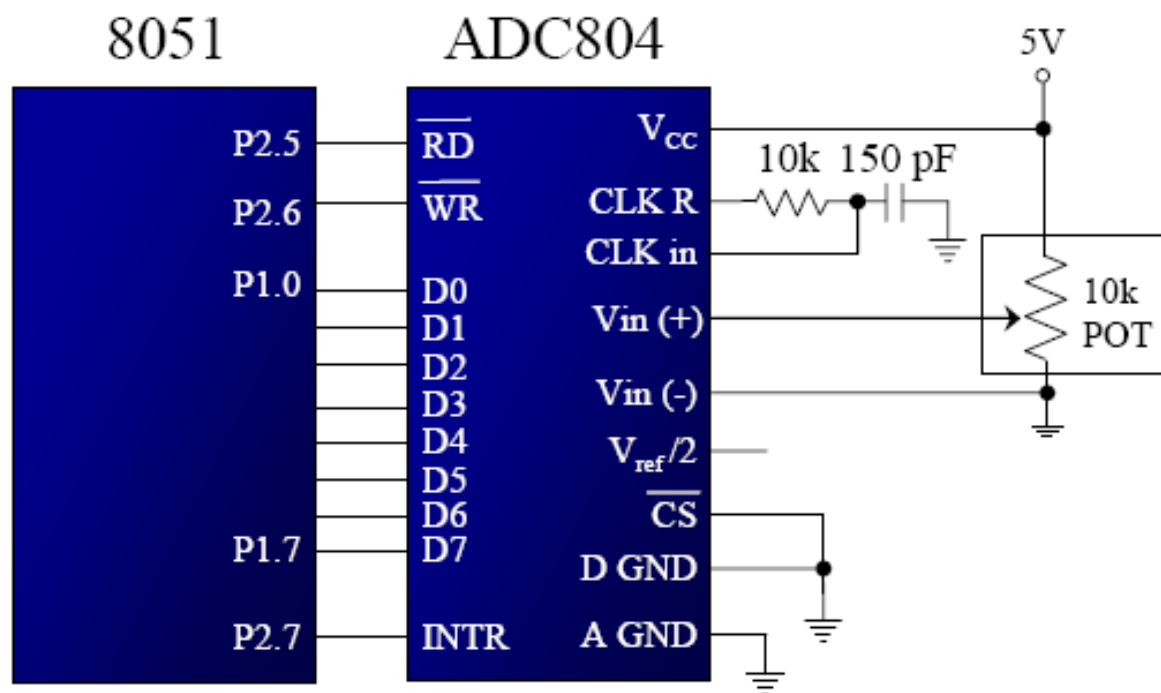
## 8051 Connection to ADC804 with Self-Clocking



Examine the ADC804 connection to the 8051 in Figure 12-7. Write a program to monitor the INTR pin and bring an analog input into register A. Then call a hex-to ASCII conversion and data display subroutines. Do this continuously.

```
;p2.6=WR (start conversion needs to L-to-H pulse)
;p2.7 When low, end-of-conversion)
;p2.5=RD (a H-to-L will read the data from ADC chip)
;p1.0 - P1.7= D0 - D7 of the ADC804
;

        RD      BIT P2.5      ;RD
        WR      BIT P2.6      ;WR (start conversion)
        INTR    BIT P2.7      ;end-of-conversion
        MYDATA  EQU P1        ;P1.0-P1.7=D0-D7 of the ADC804
        MOV     P1,#0FFH      ;make P1 = input
        SETB    INTR


BACK:   CLR     WR             ;WR=0
        SETB    WR             ;WR=1 L-to-H to start conversion
HERE:   JB      INTR,HERE     ;wait for end of conversion
        CLR     RD             ;conversion finished,enable RD
        MOV     A,MYDATA      ;read the data
        ACALL   CONVERSION    ;hex-to-ASCII conversion(Chap 6)
        ACALL   DATA_DISPLAY ;display the data(Chap 12)
        SETB    RD             ;make RD=1 for next round
        SJMP   BACK
```

# ADC808/809 Chip

- ADC808 has 8 analog inputs
  - The chip has 8-bit data output just like the ADC804
  - It allows us to monitor up to 8 different transducers using only a single chip
    - The 8 analog input channels are multiplexed and selected according to table below using three address pins, A, B, and C
- Steps to program ADC808/809
  - Select an analog channel by providing bits to A, B, and C addresses

Selected Analog Channel	C	B	A
IN0	0	0	0
IN1	0	0	1
IN2	0	1	0
IN3	0	1	1
IN4	1	0	0
IN5	1	0	1
IN6	1	1	0
IN7	1	1	1

### ADC808/809

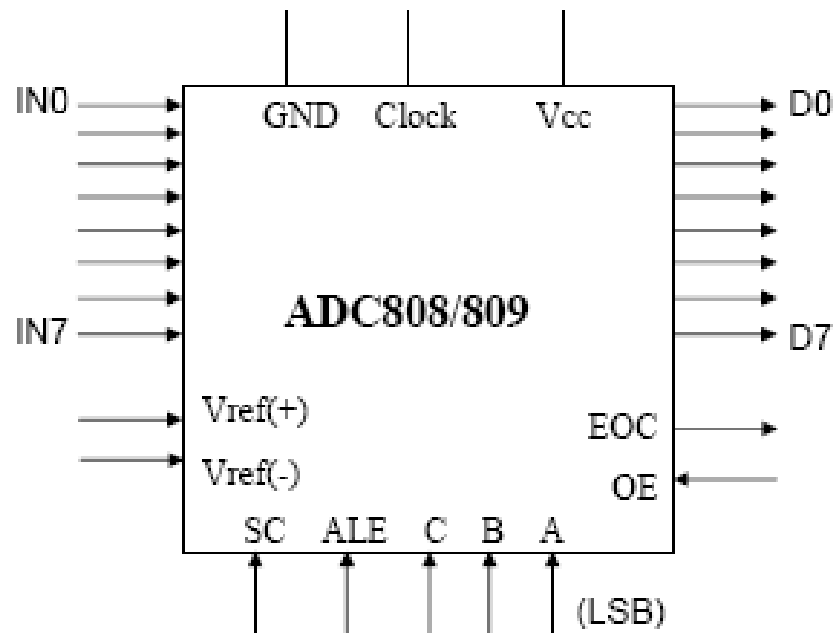



# ADC808/809 Chip (cont.)

- Activate the ALE pin
  - It needs an L-to-H pulse to latch in the address
- Activate SC (start conversion ) by an H-to-L pulse to initiate conversion
- Monitor EOC (end of conversion) to see whether conversion is finished
- Activate OE (output enable ) to read data out of the ADC chip
  - An H-to-L pulse to the OE pin will bring digital data out of the chip

# ADC0848 interfacing

The ADC0848 IC is another analog-to-digital converter in the family of the ADC0800 series from National Semiconductor Corp.

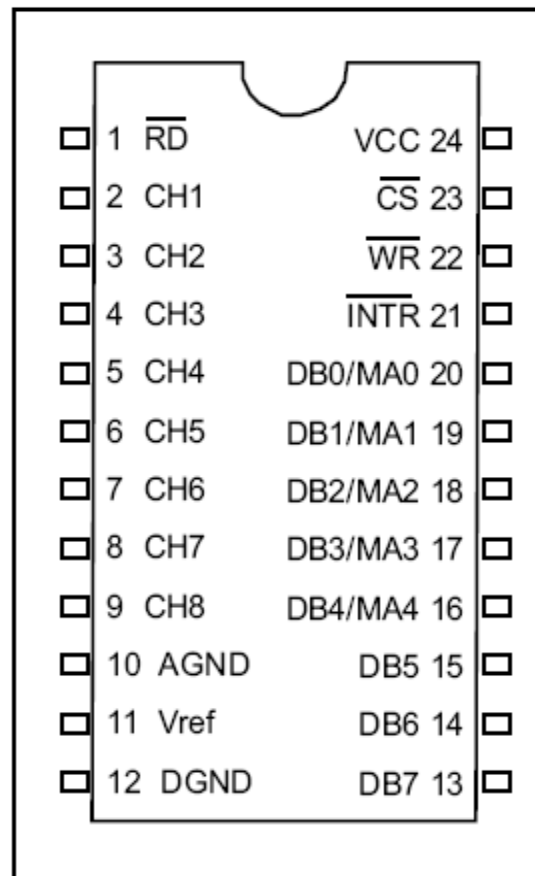


Figure 13-8. ADC0848 Chip

### Example 13-1

For a given ADC0848, we have  $V_{\text{ref}} = 2.56 \text{ V}$ . Calculate the D0 - D7 output if the analog input is: (a) 1.7 V, and (b) 2.1 V.

**Solution:**

Since the step size is  $2.56/256 = 10 \text{ mV}$ , we have the following.

(a)  $D_{\text{out}} = 1.7 \text{ V}/10 \text{ mV} = 170$  in decimal, which gives us 10101011 in binary for D7 - D0.

(b)  $D_{\text{out}} = 2.1 \text{ V}/10 \text{ mV} = 210$  in decimal, which gives us 11010010 in binary for D7 - D0.

# DAC INTERFACING

This section will show how to interface a DAC (digital-to-analog converter) to the 8051.

## Digital-to-analog (DAC) converter

The digital-to-analog converter (DAC) is a device widely used to convert digital pulses to analog signals.

## MCI408 DAC (or DAC808)

In the MCI408 (DAC0808), the digital inputs are converted to current ( $I_{out}$ ), and by connecting a resistor to the  $I_{out}$  pin, we convert the result to voltage. The total current provided by the  $I_{out}$  pin is a function of the binary numbers at the D0-D7 inputs of the DAC0808 and the reference current ( $I_{ref}$ ), and is as follows:

$$I_{out} = I_{ref} \left( \frac{D7}{2} + \frac{D6}{4} + \frac{D5}{8} + \frac{D4}{16} + \frac{D3}{32} + \frac{D2}{64} + \frac{D1}{128} + \frac{D0}{256} \right)$$

where D0 is the LSB, D7 is the MSB for the inputs, and  $I_{ref}$  is the input current that must be applied to pin 14.

### Example 13-3

Assuming that  $R = 5K$  and  $I_{ref} = 2 \text{ mA}$ , calculate  $V_{out}$  for the following binary inputs:

(a) 10011001 binary (99H)                      (b) 11001000 (C8H)

#### Solution:

(a)  $I_{out} = 2 \text{ mA} (153/256) = 1.195 \text{ mA}$  and  $V_{out} = 1.195 \text{ mA} \times 5K = 5.975 \text{ V}$

(b)  $I_{out} = 2 \text{ mA} (200/256) = 1.562 \text{ mA}$  and  $V_{out} = 1.562 \text{ mA} \times 5K = 7.8125 \text{ V}$

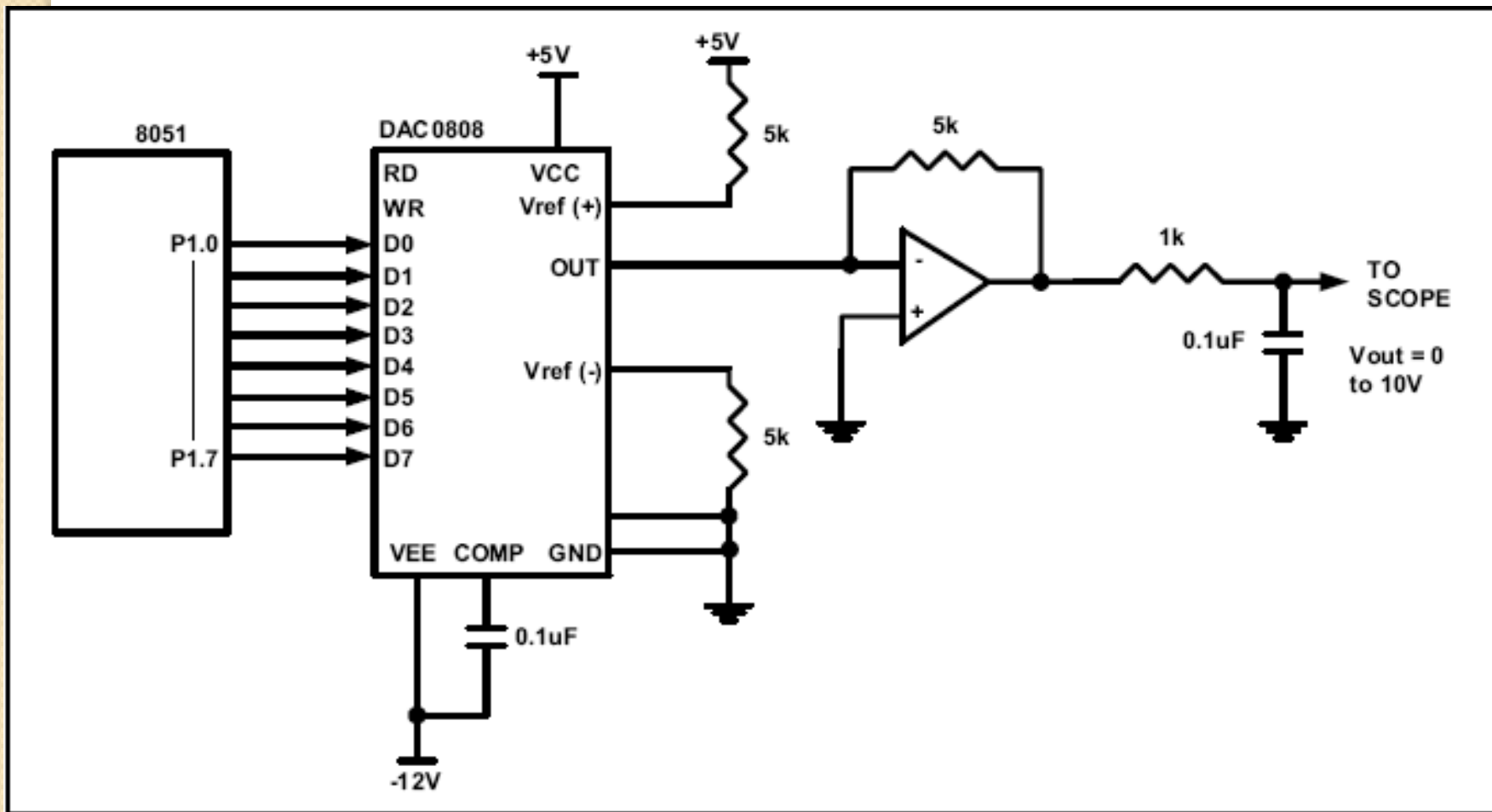


Figure 13-18. 8051 Connection to DAC808

## Generating a sine wave

To generate a sine wave, we first need a table whose values represent the magnitude of the sine of angles between 0 and 360 degrees. The values for the sine function vary from -1.0 to +1.0 for 0 – to 360- ° angles.

Therefore, to achieve the full-scale 10V output, we use the following equation.

$$V_{out} = 5 \text{ V} + (5 \times \sin \theta)$$

$V_{out}$  of DAC for various angles is calculated and shown:

**Table 13-7: Angle vs. Voltage Magnitude for Sine Wave**

<b>Angle <math>\theta</math> (degrees)</b>	<b>Sin <math>\theta</math></b>	<b><math>V_{out}</math> (Voltage Magnitude) <math>5\text{ V} + (5\text{ V} \times \sin \theta)</math></b>	<b>Values Sent to DAC (decimal) (Voltage Mag. <math>\times 25.6</math>)</b>
0	0	5	128
30	0.5	7.5	192
60	0.866	9.33	238
90	1.0	10	255
120	0.866	9.33	238
150	0.5	7.5	192
180	0	5	128
210	-0.5	2.5	64
240	-0.866	0.669	17
270	-1.0	0	0
300	-0.866	0.669	17
330	-0.5	2.5	64
360	0	5	128



### Example 13-5

Verify the values given for the following angles: (a)  $30^\circ$  (b)  $60^\circ$ .

**Solution:**

$$(a) V_{\text{out}} = 5 \text{ V} + (5 \text{ V} \times \sin \theta) = 5 \text{ V} + 5 \times \sin 30^\circ = 5 \text{ V} + 5 \times 0.5 = 7.5 \text{ V}$$

$$\text{DAC input values} = 7.5 \text{ V} \times 25.6 = 192 \text{ (decimal)}$$

$$(b) V_{\text{out}} = 5 \text{ V} + (5 \text{ V} \times \sin \theta) = 5 \text{ V} + 5 \times \sin 60^\circ = 5 \text{ V} + 5 \times 0.866 = 9.33 \text{ V}$$

$$\text{DAC input values} = 9.33 \text{ V} \times 25.6 = 238 \text{ (decimal)}$$

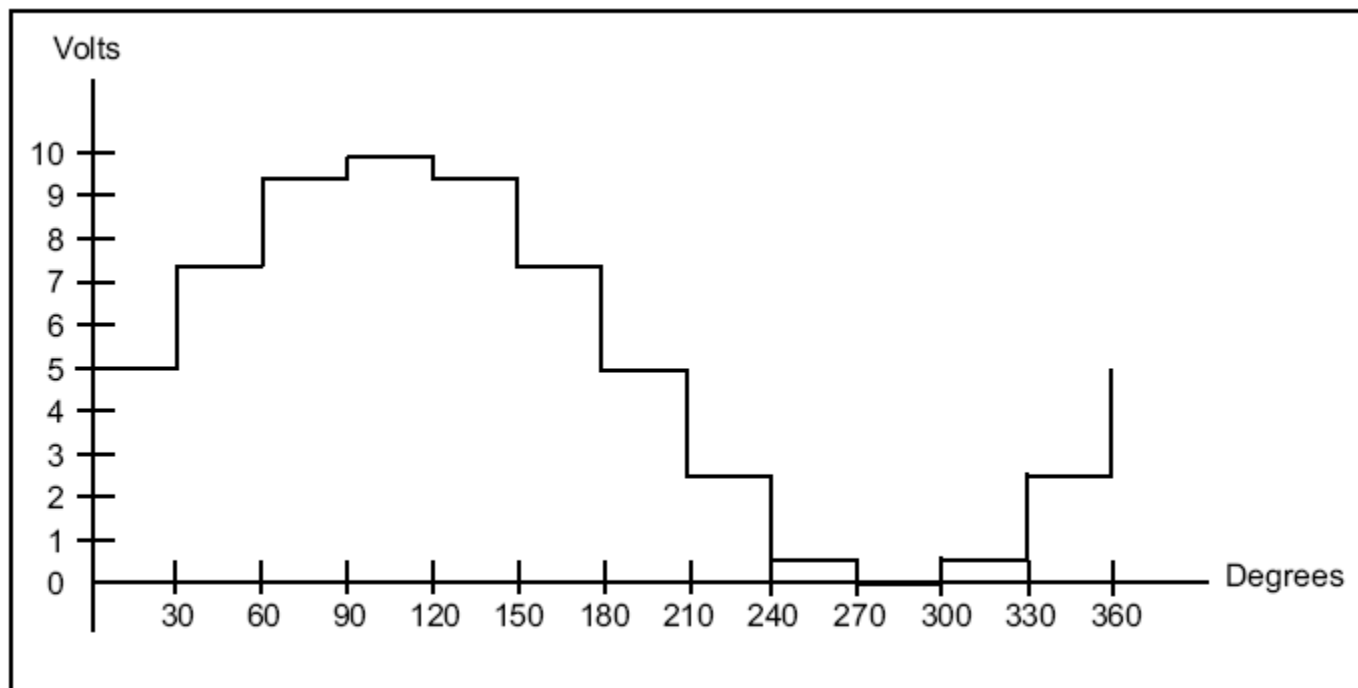


Figure 13-19. Angle vs. Voltage Magnitude for Sine Wave

This program sends the values to the DAC continuously (in an infinite loop) to produce a crude sine wave.

```
AGAIN:      MOV DPTR,#TABLE
            MOV R2,#COUNT
BACK:       CLR A
            MOVC A,@A+DPTR
            MOV P1,A
            INC DPTR
            DJNZ R2,BACK
            SJMP AGAIN
            ORG 300
TABLE:      DB 128,192,238,255,238,192 ;see Table 13-7
            DB 128,64,17,0,17,64,128
```

```
;To get a better looking sine wave, regenerate
;Table 13-7 for 2-degree angles
```

# Interfacing Temperature Sensor

- A thermistor responds to temperature change by changing resistance
  - Its response is not linear
  - The complexity associated with writing software for such nonlinear devices has led many manufacturers to market the linear temperature sensor

Temperature (C)	Tf (K ohms)
0	29.490
25	10.000
50	3.893
75	1.700
100	0.817

From William Kleitz, digital Electronics

# LM34 and LM35 Temperature Sensors

- The sensors of the LM34/LM35 series are precision integrated-circuit temperature sensors
  - The output voltage is linearly proportional to the Fahrenheit/Celsius temperature
  - The LM34/LM35 requires no external calibration since it is inherently calibrated
  - It outputs 10 mV for each degree of Fahrenheit/Celsius temperature

**Table 13-9: LM34 Temperature Sensor Series Selection Guide**

<b>Part Scale</b>	<b>Temperature Range</b>	<b>Accuracy</b>	<b>Output</b>
LM34A	-50 F to +300 F	+2.0 F	10 mV/F
LM34	-50 F to +300 F	+3.0 F	10 mV/F
LM34CA	-40 F to +230 F	+2.0 F	10 mV/F
LM34C	-40 F to +230 F	+3.0 F	10 mV/F
LM34D	-32 F to +212 F	+4.0 F	10 mV/F

*Note:* Temperature range is in degrees Fahrenheit.

**Table 13-10: LM35 Temperature Sensor Series Selection Guide**

<b>Part</b>	<b>Temperature Range</b>	<b>Accuracy</b>	<b>Output Scale</b>
LM35A	-55 C to +150 C	+1.0 C	10 mV/C
LM35	-55 C to +150 C	+1.5 C	10 mV/C
LM35CA	-40 C to +110 C	+1.0 C	10 mV/C
LM35C	-40 C to +110 C	+1.5 C	10 mV/C
LM35D	0 C to +100 C	+2.0 C	10 mV/C

*Note:* Temperature range is in degrees Celsius.

# Signal Conditioning and Interfacing LM35

- Signal conditioning is a widely used term in the world of data acquisition
  - It is the conversion of the signals (voltage, current, charge, capacitance, and resistance) produced by transducers to voltage, which is sent to the input of an A-to-D converter
    - Signal conditioning can be a current-to-voltage conversion or a signal amplification
    - The thermistor changes resistance with temperature
      - The change of resistance must be translated into voltage in order to be of any use to an ADC

## Getting Data From the Analog World

Analog world (temperature, pressure, etc. )

↓

Transducer

↓

Signal conditioning

↓

ADC

↓

Microcontroller

```
graph TD; A["Analog world (temperature, pressure, etc. )"] --> B["Transducer"]; B --> C["Signal conditioning"]; C --> D["ADC"]; D --> E["Microcontroller"];
```

### Example:


Look at the case of connecting an LM35 to an ADC804. Since the ADC804 has 8-bit resolution with a maximum of 256 steps and the LM35 (or LM34) produces 10 mV for every degree of temperature change, we can condition  $V_{in}$  of the ADC804 to produce a  $V_{out}$  of 2560 mV full-scale output. Therefore, in order to produce the full-scale  $V_{out}$  of 2.56 V for the ADC804, We need to set  $V_{ref}/2 = 1.28$ . This makes  $V_{out}$  of the ADC804 correspond directly to the temperature as monitored by the LM35.

### Temperature vs. $V_{out}$ of the ADC804

Temp. (C)	$V_{in}$ (mV)	$V_{out}$ (D7 – D0)
0	0	0000 0000
1	10	0000 0001
2	20	0000 0010
3	30	0000 0011
10	100	0000 1010
30	300	0001 1110


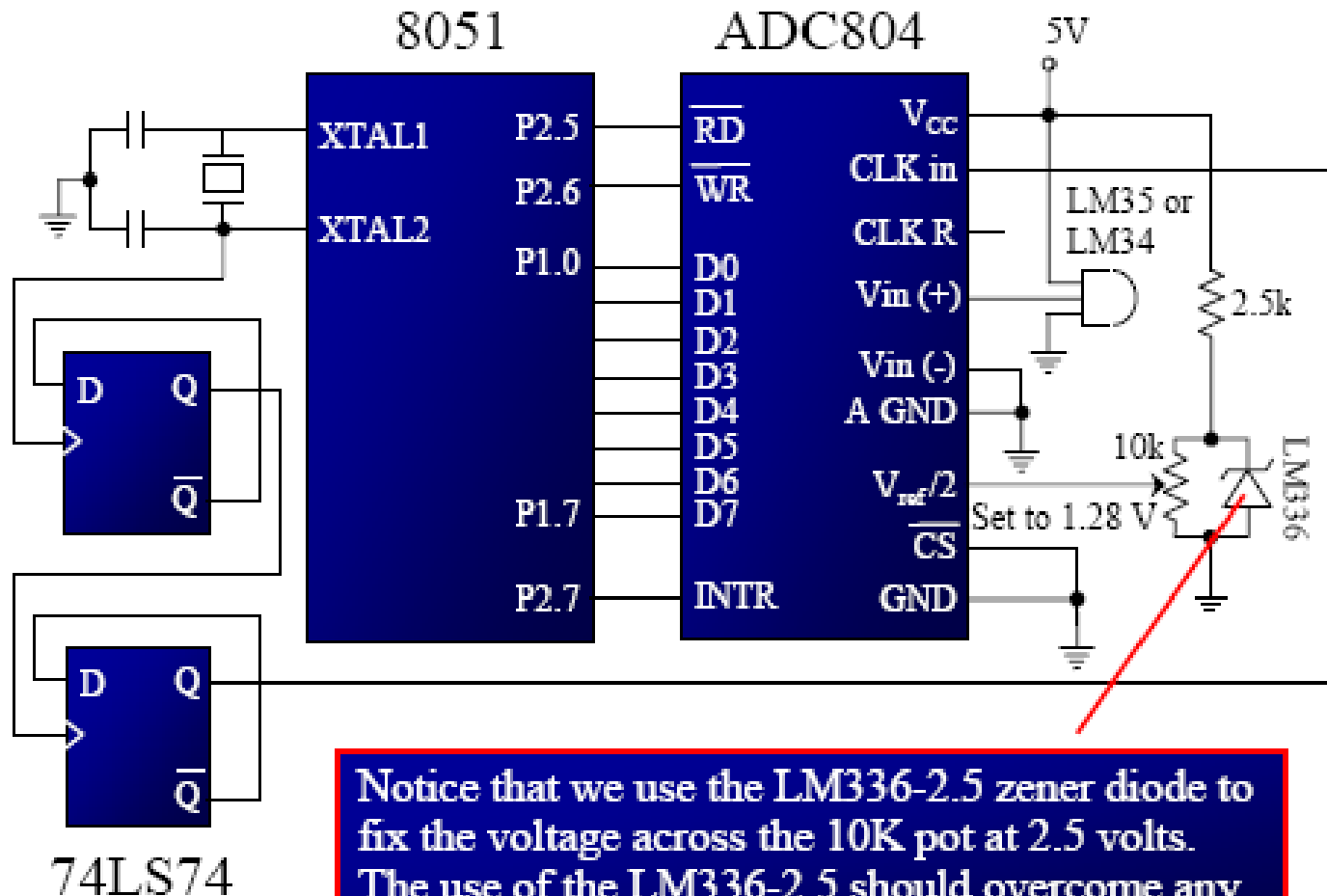
# 8051 Connection to ADC804 and Temperature Sensor



Notice that we use the LM336-2.5 zener diode to fix the voltage across the 10K pot at 2.5 volts. The use of the LM336-2.5 should overcome any fluctuations in the power supply

# Signal conditioning and interfacing the LM35 to the 8051

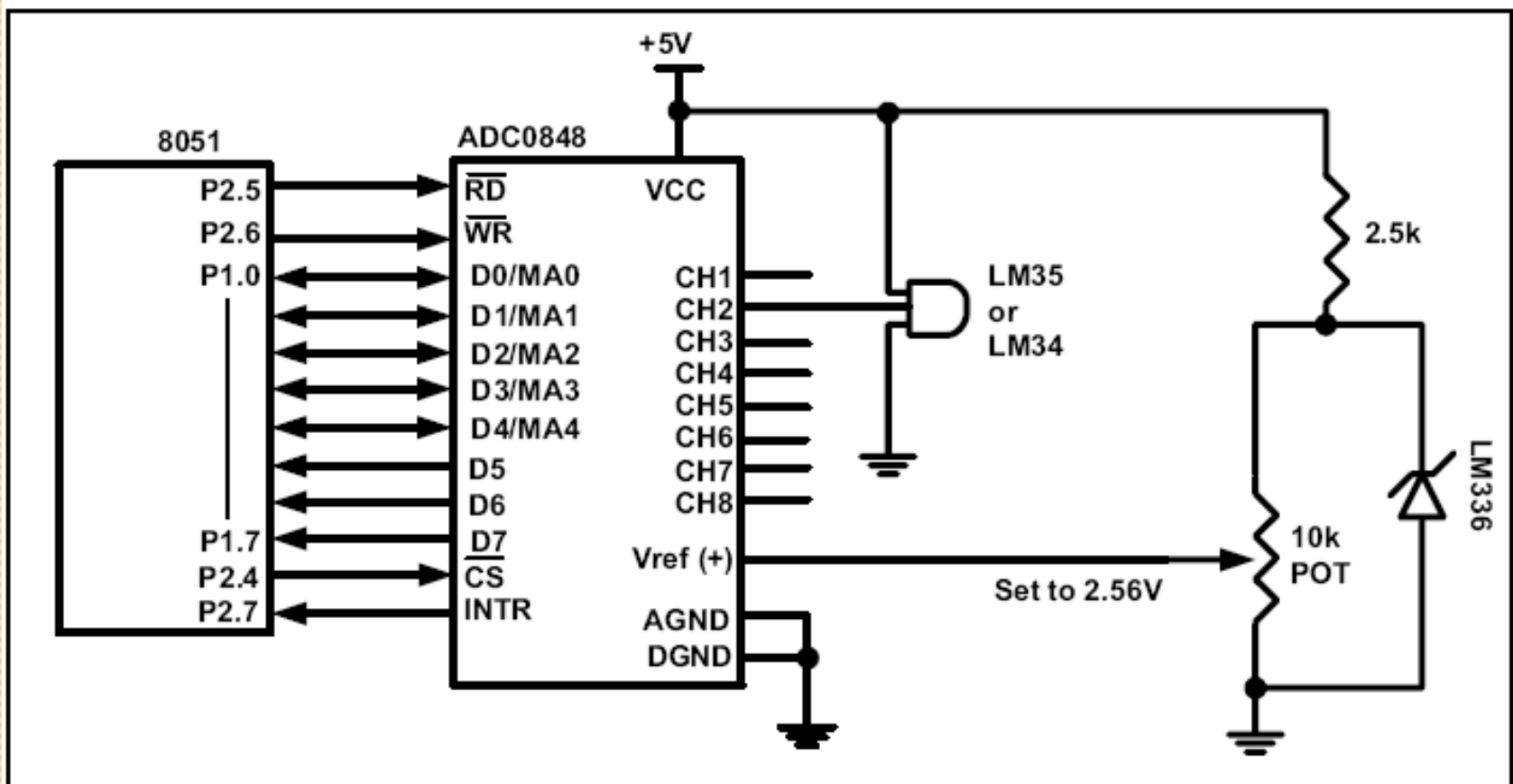


Figure 13-21. 8051 Connection to ADC0848 and Temperature Sensor

# Reading and displaying temperature

```
;Program 13-1
;Assembly code to read temperature, convert it,
;and put it on P0 with some delay
    RD    BIT P2.5           ;RD
    WR    BIT P2.6           ;WR (start conversion)
    INTR  BIT P2.7           ;end-of-conversion
    MYDATA EQU P1           ;P1.0-P1.7=D0-D7 of the ADC0848
    MOV   P1,#0FFH          ;make P1 = input
    SETB  INTR
BACK: CLR   WR               ;WR=0
      SETB  WR               ;WR=1 L-to-H to start conversion
HERE: JB   INTR,HERE        ;wait for end of conversion
      CLR   RD               ;conversion finished,enable RD
      MOV   A,MYDATA         ;read the data from ADC0848
      ACALL CONVERSION       ;hex-to-ASCII conversion
      ACALL DATA_DISPLAY    ;display the data
      SETB  RD               ;make RD=1 for next round
      SJMP  BACK
```

CONVERSION:

```
    MOV    B, #10
    DIV    AB
    MOV    R7, B           ;least significant byte
    MOV    B, #10
    DIV    AB
    MOV    R6, B
    MOV    R5, A           ;most significant byte
    RET
```

DATA\_DISPLAY

```
    MOV    P0, R7
    ACALL DELAY
    MOV    P0, R6
    ACALL DELAY
    MOV    P0, R5
    ACALL DELAY
    RET
```