

R.N.G.PATEL INSTITUTE OF TECHNOLOGY-RNGPIT
(An Autonomous College U/s UGC Act 1956)

B.Tech. SEMESTER-I, SEMESTER END EXAMINATION - WINTER 2024

Subject Code: 1EL104

Date: 21-12-2024

**Subject Name: FUNDAMENTAL OF ELECTRICAL & ELECTRONICS
ENGINEERING**

Time: 11:00 AM to 01:30 PM

Total Marks: 70

Instructions

1. It is **compulsory** for students to write **Enrolment No. /Seat No.** on the question paper.
2. Write answers of **Section A** and **Section B** in **separate answer books**.
3. Attempt all questions from both **Section A** and **Section B**.
4. Each section carries **35 marks**, with a total of **70 marks** for the examination.
5. The figures to the right of each question indicate full marks, make suitable assumptions with justification.
6. BL - Bloom's Taxonomy Levels (R-Remember, U-Understanding, A –Application, N –Analyze, E – Evaluate, C -Create), CO - Course Outcomes.

SECTION A

	Marks BL CO		
Q.1 Objective-Type Questions	[05]		
(a) Which of the following is not an expression of power?	1	R	1
(i) $P = I^2R$			
(ii) $P = VI$			
(iii) $P = V^2/R$			
(iv) $P = I/R$			
(b) The unit of resistivity is	1	R	1
(i) Ω			
(ii) Ω - metre			
(iii) Ω / metre			
(iv) Ω / m^2			
(c) The ac voltmeter or ammeter indicates the _____ value.	1	R	2
(i) Average			
(ii) RMS			
(iii) Peak			
(iv) None of these			
(d) The unit of apparent power is _____.	1	U	2
(i) Volt-amp			
(ii) VAR or KVAR			
(iii) Watt			
(iv) None of these			

- (e) The RLC series circuit is _____ if $X_L = X_C$. 1 U 2
- (i) Inductive (ii) Resistive
- (iii) Capacitive (iv) None of these

Q.2 Attempt Any Two [10]

- (a) Explain ohm's law & its limitation. 5 U 1
- (b) Explain Thevenin's theorem with its steps in brief. 5 U 1
- (c) Determine the electricity bill amount for a month of April, if 4 bulbs of 40 W for 5 hrs. 4 tube lights of 60 W for 5 hrs. A TV of 100 W for 6 hrs. A washing machine of 400 W for 3 hrs. A water pump of 0.5 HP for 15 minutes are used per day. The cost per unit is Rs. 3.50. Consider 1 HP = 746 watts. 5 E 1

Q.3 Attempt Any Two [10]

- (a) Define following terms in connection with A.C wave forms: (i) Time Period 5 R 2
(ii) Frequency (iii) Power Factor (iv) Form Factor (v) Average Value.
- (b) Determine the current & average power equation for Pure Inductive AC circuit and draw voltage and current waveform. 5 E 2
- (c) Compare series resonance and parallel resonance. 5 U 2

Q.4 Attempt Any Two [10]

- (a) Explain Construction, Working of solar cell and also write advantage and disadvantage. 5 A 5
- (b) Explain Construction and Working of BJT. 5 A 5
- (c) Give the difference between MOSFET and JFET. 5 U 5

SECTION B

	Marks	BL	CO
Q.5 Objective-Type Questions	[05]		
(a) Elimination of a hole and a free electron is called as _____ (i) carrier generation (ii) carrier recombination (iii) carrier generation and carrier recombination (iv) none of these	1	U	4
(b) For Intrinsic semiconductors, the Fermi level lies _____ (i) near the valance band (ii) near the conduction band (iii) in the middle of forbidden band (iv) all of these.	1	U	3
(c) The Fermi level of Extrinsic semiconductor depends on _____ (i) temperature (ii) concentration of impurity (iii) both (i) and (ii) (iv) none of these	1	U	3
(d) Which of the following impurity is used to make P –type semiconductor? (i) P (ii) As (iii) Al (iv) Sb	1	U	3
(e) Temperature coefficient of semiconductor is _____ (i) positive (ii) negative (iii) zero (iv) infinite	1	U	3
Q.6 Attempt Any Two	[10]		
(a) Explain extrinsic semiconductor in details.	5	U	3
(b) At what temperature we can expect 45% Fermi probability function when the energy level is lying 0.02eV above its Fermi level?	5	A	3
(c) Describe the Pulling technique for the crystal growth in detail.	5	U	3
Q.7 Attempt Any Two	[10]		
(a) Explain Construction, Working and IV characteristics of PN Junction diode.	5	U	4
(b) Explain Full Wave rectifier in detail.	5	A	4
(c) Describe in detail Principle, Construction and Working of ZENER Diode.	5	U	4

Q.8 Attempt Any Two

[10]

- | | | | |
|--|----------|----------|----------|
| (a) Describe in detail construction, working and IV characteristics of LED. | 5 | U | 4 |
| (b) Describe principle, construction, working of Schottky diode and list out application. | 5 | U | 4 |
| (c) Write down the difference between conductor, semiconductor and insulator. | 5 | U | 3 |
