

R.N.G.PATEL INSTITUTE OF TECHNOLOGY-RNGPIT
(An Autonomous Institute U/s UGC Act 1956)

B.Tech. SEMESTER-I, SEMESTER END EXAMINATION – WINTER 2025

SUBJECT CODE: 1EL104

DATE: 22-12-2025

**SUBJECT NAME: FUNDAMENTAL OF ELECTRICAL AND
ELECTRONICS ENGINEERING**

TIME: 11:00 AM to 01:30 PM

TOTAL MARKS: 70

Instructions

1. It is **compulsory** for students to write **Enrolment No. /Seat No.** on the question paper.
2. Write answers of **Section A** and **Section B** in **separate answer books**.
3. Attempt all questions from both **Section A** and **Section B**.
4. Each section carries **35 marks**, with a total of **70 marks** for the examination.
5. The figures to the right of each question indicate full marks, make suitable assumptions with justification.
6. BL - Bloom's Taxonomy Levels (R-Remember, U-Understanding, A –Application, N –Analyze, E – Evaluate, C -Create), CO - Course Outcomes.

SECTION A

	Marks	BL	CO				
Q.1 Multiple-Choice Questions	[05]						
(a) The unit of resistivity is	1	R	1				
<table style="width: 100%; border: none;"> <tr> <td style="width: 50%; padding: 5px 0;">(i) Ω</td> <td style="width: 50%; padding: 5px 0;">(ii) Ω - metre</td> </tr> <tr> <td style="padding: 5px 0;">(iii) Ω / metre</td> <td style="padding: 5px 0;">(iv) Ω / m²</td> </tr> </table>	(i) Ω	(ii) Ω - metre	(iii) Ω / metre	(iv) Ω / m ²			
(i) Ω	(ii) Ω - metre						
(iii) Ω / metre	(iv) Ω / m ²						
(b) Power factor in purely resistive circuit?	1	R	2				
<table style="width: 100%; border: none;"> <tr> <td style="width: 50%; padding: 5px 0;">(i) Zero</td> <td style="width: 50%; padding: 5px 0;">(ii) Both</td> </tr> <tr> <td style="padding: 5px 0;">(iii) Unity</td> <td style="padding: 5px 0;">(iv) None of these</td> </tr> </table>	(i) Zero	(ii) Both	(iii) Unity	(iv) None of these			
(i) Zero	(ii) Both						
(iii) Unity	(iv) None of these						
(c) The average power in purely capacitive circuit is	1	R	2				
<table style="width: 100%; border: none;"> <tr> <td style="width: 50%; padding: 5px 0;">(i) Unity</td> <td style="width: 50%; padding: 5px 0;">(ii) Zero (leading)</td> </tr> <tr> <td style="padding: 5px 0;">(iii) Zero (lagging)</td> <td style="padding: 5px 0;">(iv) None of these</td> </tr> </table>	(i) Unity	(ii) Zero (leading)	(iii) Zero (lagging)	(iv) None of these			
(i) Unity	(ii) Zero (leading)						
(iii) Zero (lagging)	(iv) None of these						
(d) The main material used in a solar cell is	1	R	5				
<table style="width: 100%; border: none;"> <tr> <td style="width: 50%; padding: 5px 0;">(i) Copper</td> <td style="width: 50%; padding: 5px 0;">(ii) Silicon</td> </tr> <tr> <td style="padding: 5px 0;">(iii) Iron</td> <td style="padding: 5px 0;">(iv) Nickel</td> </tr> </table>	(i) Copper	(ii) Silicon	(iii) Iron	(iv) Nickel			
(i) Copper	(ii) Silicon						
(iii) Iron	(iv) Nickel						

- (e) FETs are widely used because they have 1 R 5
- (i) High power loss (ii) High input impedance
- (iii) Low input impedance (iv) High noise

- Q.2 Attempt Any Two** [10]
- (a) Explain KCL and KVL. 5 U 1
- (b) Explain Thevenin's theorem with its steps in brief. 5 U 1
- (c) Calculate the electricity bill amount for a month of April, if 4 bulbs of 40 W for 5 h, 4 tube lights of 60 W for 5 h, a TV of 100 W for 6 h, a washing machine of 400 W for 3 h, a water pump of 0.5 HP for 15 minutes are used per day. The cost per unit is Rs 3.50. Consider 1 HP = 746 watts. 5 R 1
- Q.3 Attempt Any Two** [10]
- (a) Define following terms in connection with A.C wave forms: 5 R 2
- (i) Frequency (ii) Form Factor (iii) R. M. S. Value (iv) Amplitude (v) Peak Factor
- (b) Compare series and parallel resonance. 5 U 2
- (c) Explain the current in purely inductive circuit leads its voltage by 90° and average power consumption in pure inductor is zero. 5 U 2
- Q.4 Attempt Any Two** [10]
- (a) List out types of FETs and explain its operation. 5 R 5
- (b) Explain structure and operation of BJT. 5 U 5
- (c) Explain principle and working of solar cells. 5 U 5

SECTION B

	Marks	BL	CO				
Q.5 Multiple-Choice Questions	[05]						
(a) Which of the following, when added as an impurity, into the silicon, produces n-type semiconductor?	1	R	3				
<table border="0" style="width: 100%;"> <tr> <td style="width: 50%;">(i) Phosphorous</td> <td style="width: 50%;">(ii) Aluminum</td> </tr> <tr> <td>(iii) Magnesium</td> <td>(iv) Sulfur</td> </tr> </table>	(i) Phosphorous	(ii) Aluminum	(iii) Magnesium	(iv) Sulfur			
(i) Phosphorous	(ii) Aluminum						
(iii) Magnesium	(iv) Sulfur						
(b) What are the charge carriers in semiconductors?	1	R	3				
<table border="0" style="width: 100%;"> <tr> <td style="width: 50%;">(i) Electrons and holes</td> <td style="width: 50%;">(ii) Electrons</td> </tr> <tr> <td>(iii) Holes</td> <td>(iv) Charges</td> </tr> </table>	(i) Electrons and holes	(ii) Electrons	(iii) Holes	(iv) Charges			
(i) Electrons and holes	(ii) Electrons						
(iii) Holes	(iv) Charges						
(c) In the zone melting method _____ of the charge is melted at any one time.	1	R	3				
<table border="0" style="width: 100%;"> <tr> <td style="width: 50%;">(i) Small part</td> <td style="width: 50%;">(ii) Large part</td> </tr> <tr> <td>(iii) Solid part</td> <td>(iv) Anionic part</td> </tr> </table>	(i) Small part	(ii) Large part	(iii) Solid part	(iv) Anionic part			
(i) Small part	(ii) Large part						
(iii) Solid part	(iv) Anionic part						
(d) Which column elements are combined to make compound semiconductors?	1	U	3				
<table border="0" style="width: 100%;"> <tr> <td style="width: 50%;">(i) Fifth and sixth</td> <td style="width: 50%;">(ii) Second and fourth</td> </tr> <tr> <td>(iii) First and fourth</td> <td>(iv) Third and fifth</td> </tr> </table>	(i) Fifth and sixth	(ii) Second and fourth	(iii) First and fourth	(iv) Third and fifth			
(i) Fifth and sixth	(ii) Second and fourth						
(iii) First and fourth	(iv) Third and fifth						
(e) What type of material is obtained when an intrinsic semiconductor is doped with trivalent impurity?	1	U	3				
<table border="0" style="width: 100%;"> <tr> <td style="width: 50%;">(i) P-type semiconductor</td> <td style="width: 50%;">(ii) N-type semiconductor</td> </tr> <tr> <td>(iii) Insulator</td> <td>(iv) Conductor</td> </tr> </table>	(i) P-type semiconductor	(ii) N-type semiconductor	(iii) Insulator	(iv) Conductor			
(i) P-type semiconductor	(ii) N-type semiconductor						
(iii) Insulator	(iv) Conductor						
Q.6 Attempt Any Two	[10]						
(a) Write difference between intrinsic semiconductor and extrinsic semiconductor.	5	U	3				
(b) Explain Czochralski process of crystal growth in detail.	5	U	3				
(c) Write difference between Conductors, Semiconductors and Insulators.	5	U	3				
Q.7 Attempt Any Two	[10]						
(a) What is PN junction? Describe its forward and reverse biasing.	5	R	4				
(b) Write a short note on LED.	5	R	4				

(c) Explain Full wave rectifier with appropriate diagram. **5 R 4**

Q.8 Attempt Any Two [10]

(a) Explain half wave rectifier with appropriate diagram. **5 U 4**

(b) Explain construction and working of Schottky diode. **5 U 4**

(c) Write a short note on drift and diffusion. **5 U 4**
