

R.N.G.PATEL INSTITUTE OF TECHNOLOGY-RNGPIT
(An Autonomous Institute U/s UGC Act 1956)

B.Tech. SEMESTER-III, SEMESTER END EXAMINATION – WINTER 2025

SUBJECT CODE: 1EL304

DATE: 23-12-2025

SUBJECT NAME: ANALOG AND DIGITAL ELECTRONICS

TIME: 11:00 AM to 01:30 PM

TOTAL MARKS: 70

Instructions

1. It is **compulsory** for students to write **Enrolment No. /Seat No.** on the question paper.
2. Write answers of **Section A** and **Section B** in **separate answer books**.
3. Attempt all questions from both **Section A** and **Section B**.
4. Each section carries **35 marks**, with a total of **70 marks** for the examination.
5. The figures to the right of each question indicate full marks, make suitable assumptions with justification.
6. BL - Cognitive Level (As per Revised Bloom's Taxonomy) (R-Remember, U-Understanding, A –Application, N –Analyze, E – Evaluate, C -Create), CO - Course Outcomes.

SECTION A

		Marks	BL	CO
Q.1	(a) What is comparator? Explain the use of op-amp as a zero crossing detector.	03	R	3
	(b) Explain working of Schmitt trigger with necessary circuit diagram & Waveforms.	04	U	3
Q.2	(a) Illustrate Difference between combinational logic circuit and sequential logic circuit.	03	U	5
	(b) Show the operation of S-R Flip-Flop with circuit diagram and truth table.	04	R	5
	(c) Construct serial in parallel out shift register, explain its working also give classification of the various types of shift registers.	07	A	5
OR				
Q.2	(a) Illustrate Difference between level triggering and edge triggering of flip-flops.	03	U	5
	(b) Show the operation of J-K Flip-Flop with circuit diagram and truth table.	04	R	5
	(c) Build 4 – bit synchronous up - counter (Use T flip-flop).	07	A	5
Q.3	(a) Define following specifications of DAC: Resolution, Accuracy, Settling time	03	R	6
	(b) Explain sample and hold circuit.	04	U	6
	(c) Explain D/A converter with binary weighted resistors.	07	U	6

OR

Q.3	(a) List the applications of DAC and ADC.	03	R	6
	(b) Compare various DAC techniques.	04	U	6
	(c) Explain working of successive-approximation register A/D converter.	07	U	6

SECTION B

		Marks	BL	CO
Q.4	(a) Define an operational amplifier and list its ideal characteristics.	03	U	1
	(b) Explain the working of a differential amplifier and its importance in the input stage of an op-amp.	04	N	1
Q.5	(a) Draw and explain the working of an inverting amplifier using op-amp.	03	U	2
	(b) Describe the Wien bridge oscillator using an op-amp with a diagram and give its frequency formula.	04	U	2
	(c) What is an instrumentation amplifier? Explain its construction and derive the formula for total gain.	07	R	2
OR				
Q.5	(a) Draw and explain the working of a non-inverting amplifier using op-amp with a neat diagram.	03	U	2
	(b) Explain the operation of a differential amplifier and state its applications.	04	U	2
	(c) Explain the op-amp differentiator circuit. Derive the output voltage equation and discuss its practical limitations.	07	R	2
Q.6	(a) Simplify the Boolean expression using Boolean algebra: $F=A'B+AB'+AB$	03	A	4
	(b) Design a 2 to 4 decoder and explain its working with a logic diagram.	04	A	4
	(c) Design and explain an 4-to-1 multiplexer using logic gates.	07	E	4

OR

Q.6	(a) Apply your knowledge of digital logic to explain the function and application of a digital comparator.	03	A	4
	(b) Simplify the Boolean function $F(A,B,C)=\Sigma(1,2,3,5,7)$ using K-map.	04	A	4
	(c) Design a binary-to-Gray code converter using logic gates and explain its working with truth table.	07	E	4
